
Lecture 6: HDL V

ECE 228


Mostafizur Rahman
rahmanmo@umkc.edu

Behavioral Model - Procedures (i)

- The procedural block defines
 - A region of code containing sequential statements
 - The statements execute in the order they are written
- Procedures: sections of code that we know they execute sequentially
- Procedural statements: statements inside a procedure (they execute sequentially)
- Two types of procedural blocks in Verilog
 - The “always” block
 - A continuous loop that never terminates
 - The “initial” block
 - Executed once at the beginning of simulation (used in Test-benches for the purpose of verification)

Behavioral Model - Procedures (ii)
 
```
always @ (event_expression)
begin
statement;
.....
.....
statement;
end
```



- Modules can contain any number of procedures
- Procedures execute in parallel (in respect to each other) and ..

Assignment

- Continuous assignment
 - Values are assigned to net variables due to some input variable changes
 - “**assign** ...=...”
- Procedural assignment
 - Procedural assignment is used to assign value to variables. A variable cannot be a net type signal
 - Values are assigned to register variables when certain statement is executed in a behavioral description
 - Procedural assignment, “**=**”
 - Variable assignments must be in behavioral blocks.
- Difference between continuous assignment and procedural assignment
 - Continuous assignment changes the value of the target net whenever the right-hand-side operands change value.
 - Procedural assignment changes the target register only when the assignment is executed according to the sequence of operations

An initial Block Example

- Executes exactly once during simulation
- Starts at simulation time 0

```
reg x, y, z;  
initial begin    // complex statement  
    x = 1`b0; y = 1`b1; z = 1`b0;  
#10    x = 1`b1; y = 1`b1; z = 1`b1;  
end  
initial x = 1`b0; // single statement
```

An always Block Example

- Starts at simulation time 0
- Executes continuously during simulation

```
reg clock;  
initial clock = 1`b0;  
  
always #5 clock = ~clock;
```

Event control statements

- An event occurs when a net or register changes its value. The event can be further specified as a rising edge (by **posedge**) or falling edge (by **negedge**) of a signal.

- `@`
 `always @(signal1 or signal2 or ..) begin`
 `..`
 `end`

execution triggers every
time any signal changes

`always @(posedge clk) begin`
 `..`
 `end`

execution triggers every
time clk changes
from 0 to 1

`always @(negedge clk) begin`
 `..`
 `end`

execution triggers every
time clk changes
from 1 to 0

Event Control

- Event Control
 - Edge Triggered Event Control
 - Level Triggered Event Control

- Edge Triggered Event Control

@ (posedge CLK) //Positive Edge of CLK

Curr_State = Next_state;

| @ negedge | @ posedge |
|-----------|-----------|
| 1 → x | 0 → x |
| 1 → z | 0 → z |
| 1 → 0 | 0 → 1 |
| x → 0 | x → 1 |
| z → 0 | z → 1 |

- Level Triggered Event Control

@ (A or B) //change in values of A or B

Out = A & B;

Activity- Draw Timing Diagrams and Correct

- half adder implementation

```
module half_adder(S, C, A, B);  
  output S, C;  
  input A, B;  
  
  reg S,C;  
  wire A, B;  
  
  always @(A or B) begin  
    S = A && B;  
    C = A ^ B;  
  end  
  
endmodule
```

- Behavioral edge-triggered DFF implem

```
module dff(Q, D, Clk);  
  output Q;  
  input D, Clk;  
  
  reg Q;  
  wire D, Clk;  
  
  always @(posedge D)  
    Q = D;  
  
endmodule
```

Notice outputs?

Procedural Statements: if

```
if (expr1)
    true_stmt1;

else if (expr2)
    true_stmt2;

..

else
    def_stmt;
```

E.g. 4-to-1 mux:

```
module mux4_1(out, in, sel);
    output out;
    input [3:0] in;
    input [1:0] sel;

    reg out;
    wire [3:0] in;
    wire [1:0] sel;

    always @(in or sel)
        if (sel == 0)
            out = in[0];
        else if (sel == 1)
            out = in[1];
        else if (sel == 2)
            out = in[2];
        else
            out = in[3];
endmodule
```

Activity

- Write behavioral code for 4:1 multiplexer, with 4 inputs (A, B, C) each 1 bit and selects (S0, S1). Starting value for select should be 11

Example of Flip-flop

```
module Flip_flop ( q, data_in, clk, rst );  
  input          data_in, clk, rst;  
  output         q;  
  reg  q;
```

```
  always @ ( posedge clk )
```

← *Declaration of synchronous behavior*

```
  begin
```


```
    if ( rst == 1) q = 0;
```

```
    else q = data_in;
```


```
  end
```

```
endmodule
```

← *Procedural statement*

 

Example

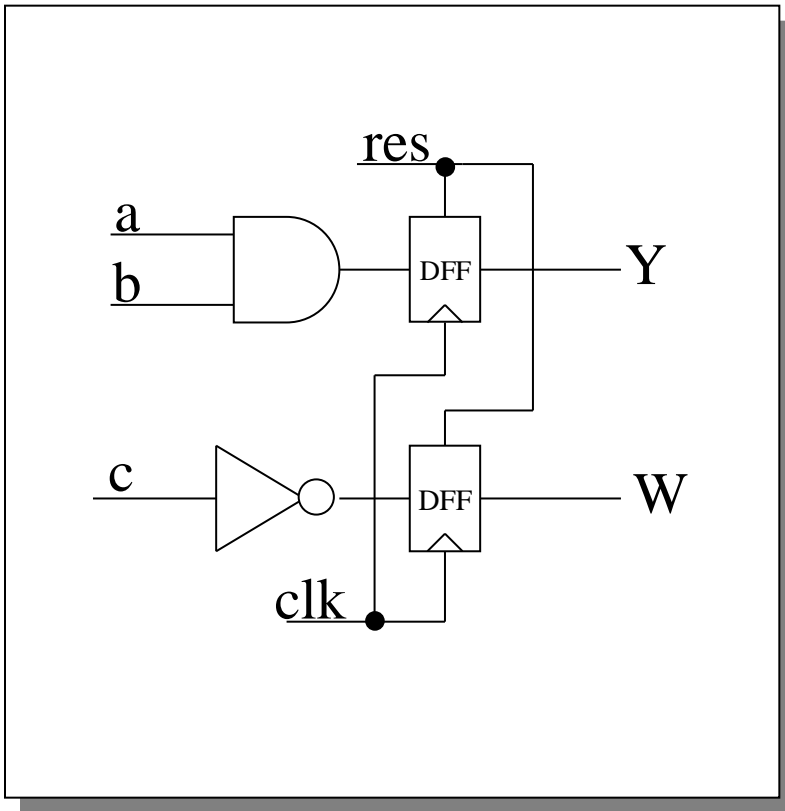

```
always @(res or posedge clk) begin
    if (res) begin
        Y = 0;
        W = 0;
    end
    else begin
        Y = a & b;
        W = ~c;
    end
end
```

What is the corresponding circuit implementation?

Conditional Statements - if ... else

- **if Statement**

- Format:


```
if (condition)
    procedural_statement
else if (condition)
    procedural_statement
else
    procedural_statement
```

- Example:

```
if (Clk)
    Q = 0;
else
    Q = D;
```

Mixed Model

 Code that contains various both structure and behavioral styles



```
module simple(Y, c, clk, res);  
output Y;  
input c, clk, res;
```

```
reg Y;  
wire c, clk, res;  
wire n;
```

```
not(n, c); // gate-level
```

```
always @(res or posedge clk)  
    if (res)  
        Y = 0;  
    else  
        Y = n;  
endmodule
```

Any other examples?

Procedural Assignment with always


- Procedural and continues assignments can co-exist within a module
- Procedural assignments update the *reg* value. The value remains unchanged till another procedural assignment updates the variable.

```
module mux_2_to_1(a, b, out,  
                  outbar, sel);  
  input a, b, sel;  
  output out, outbar;  
  reg out;
```

```
  always @ (a or b or sel)  
  begin  
    if (sel) out = a;  
    else out = b;  
  end
```

```
  assign outbar = ~out;
```

```
endmodule
```

 

*procedural
description*

*continuous
description*

The Case Statement

- Case statements:

```
case (<expression>)
  <value1>: <statement>
  <value2>: <statement>
  .....
default: <statement>
endcase
```

- case* and *if* may be used interchangeably to implement conditional execution within *always* blocks
- case* is easier to read than a long string of *if* then *else* statements

```
module mux_2_to_1(a, b, out,
                  outbar, sel);
  input a, b, sel;
  output out, outbar;
  reg out;

  always @ (a or b or sel)
  begin
    if (sel) out = a;
    else out = b;
  end


  assign outbar = ~out;
endmodule
```

```
module mux_2_to_1(a, b, out,
                  outbar, sel);
  input a, b, sel;
  output out, outbar;
  reg out;

  always @ (a or b or sel)
  begin
    case (sel)
      1'b1: out = a;
      1'b0: out = b;
    endcase
  end
endmodule
```

Danger of Incomplete Specification

Goal:

 

3-to-1 MUX

('11' input is a don't-care)

Proposed Verilog Code:

```
module maybe_mux_3to1(a, b, c,
                      sel, out);

    input [1:0] sel;
    input a,b,c;
    output out;
    reg out;

    always @(a or b or c or sel)
    begin
        case (sel)
            2'b00: out = a;
            2'b01: out = b;
            2'b10: out = c;
        endcase
    end
endmodule
```

Is this a 3-to-1 multiplexer?


Incomplete Specifications

- Incomplete Specification Infers Latches

```
module maybe_mux_3to1(a, b, c,  
                      sel, out);  
  
  input [1:0] sel;  
  input a,b,c;  
  output out;  
  reg out;  
  
  always @(a or b or c or sel)  
  begin  
    case (sel)  
      2'b00: out = a;  
      2'b01: out = b;  
      2'b10: out = c;  
    endcase  
  end  
endmodule
```

if out is not assigned
during any pass through
the always block, then **the
previous value must be
retained!**

Synthesized Result:

 

- Latch memory “latches” old data when $G=0$
- In practice, we almost *never* intend this

Avoiding Incomplete Specification

- Precede all the conditional statements with a default assignment for all signals assigned within them

```
always @(a or b or c or sel)
begin
    out = 1'bx;
    case (sel)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
    endcase
end
endmodule
```

- Or fully specify all the branches of conditional statements and assign all signals from all branches
 - For each *if*, include *else*
 - For each *case*, include *default*

```
always @(a or b or c or sel)
begin
    case (sel)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
        default: out = 1'bx;
    endcase
end
endmodule
```

Behavioral : 4-input Multiplexer

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
```

```
    reg out;
```

```
    always @( a or b or c or d or sel )
```

```
    begin
```

```
        if ( sel == 0 )
```

```
            out = a;
```

```
        else if ( sel == 1 )
```

```
            out = b
```

```
        else if ( sel == 2 )
```

```
            out = c
```

```
        else if ( sel == 3 )
```

```
            out = d
```

```
    end
```

```
endmodule
```

An always block is a behavioral block which contains a list of expressions which are (usually) evaluated sequentially

The code in an always block can be very abstract (similar to C code) - here we implement a mux with an if/else statement

Behavioral : 4-input Multiplexer

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
```


```
    reg out;
```

```
    always @( a or b or c or d or sel )
    begin
```

```
        if ( sel == 0 )
            out = a;
        else if ( sel == 1 )
            out = b;
        else if ( sel == 2 )
            out = c;
        else if ( sel == 3 )
            out = d;
```

```
    end
```

```
endmodule
```

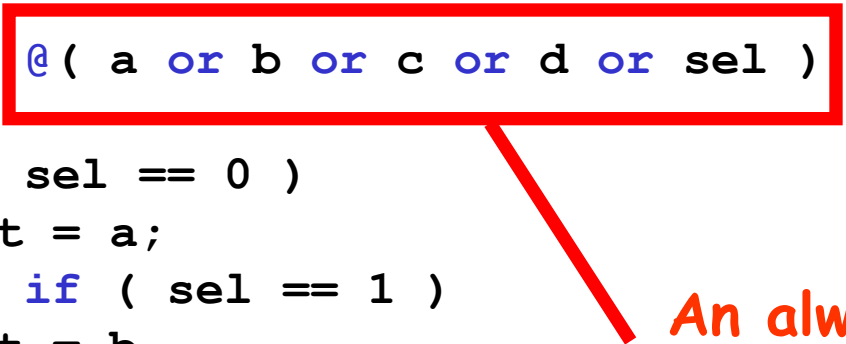

An always block can include a sensitivity list - if any of these signals change then the always block is executed

Behavioral : 4-input Multiplexer

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
```

```
    reg out;
```

```
    always @( a, b, c, d, sel )
    begin
```

```
        if ( sel == 0 )
```

```
            out = a;
```

```
        else if ( sel == 1 )
```

```
            out = b
```

```
        else if ( sel == 2 )
```

```
            out = c
```

```
        else if ( sel == 3 )
```

```
            out = d
```

```
    end
```

```
endmodule
```



In Verilog-2001 we can use a comma instead of the or

Behavioral : 4-input Multiplexer

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
```

```
    reg out;
```

```
    always @( a, b, c, d, sel )
    begin
```

```
        if ( sel == 0 )
```

```
            out = a;
```

```
        else if ( sel == 1 )
```

```
            out = b
```

```
        else if ( sel == 2 )
```

```
            out = c
```

```
        else if ( sel == 3 )
```

```
            out = d
```

```
    end
```

```
endmodule
```

What happens if we accidentally
leave off a signal on the
sensitivity list?

The always block will not
execute if just d changes - so if
sel == 3 and d changes then
out will not be updated

Behavioral : 4-input Multiplexer

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
```

```
    reg out;
```

```
    always @( * )
```

```
    begin
```

```
        if ( sel == 2'b00 )
```

```
            out = a;
```

```
        else if ( sel == 2'b01 )
```

```
            out = b
```

```
        else if ( sel == 2'b10 )
```

```
            out = c
```

```
        else if ( sel == 2'b11 )
```

```
            out = d
```

```
    end
```

```
endmodule
```

In Verilog-2001 we can use the `@(*)` construct which creates a sensitivity list for all signals read in the always block

Sequential *always* Block


- Edge triggered circuits are described using a sequential *always* block

Combinational

```
module combinational(a, b, sel,
                    out);

    input a, b;
    input sel;
    output out;
    reg out;

     always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;
    end
endmodule
```




Sequential

```
module sequential(a, b, sel,
                 clk, out);

    input a, b;
    input sel, clk;
    output out;
    reg out;

     always @ (posedge clk)
    begin
        if (sel) out <= a;
        else out <= b;
    end
endmodule
```



Blocking & Non-blocking Assignments

- Sequential statements within procedural blocks (“always” and “initial”) can use two types of assignments:
 - Blocking assignment: A blocking statement must be executed before the execution of the statements that follow it in a sequential block.
 - Uses the ‘=’ operator
 - Strict order of execution; block the assignments that follows
 - Recommended style for modeling combinational circuit
 - Non-blocking assignment: Allows to schedule assignments without blocking the procedural flow. Can make several register assignments within the same time step irrespective of the statements order or dependence upon each other.
 - Uses the ‘<=’ operator
 - Recommended style for modeling sequential circuit

Blocking vs. Nonblocking Assignments

- Verilog supports two types of assignments within `always` blocks, with subtly different behaviors.
- **Blocking assignment:** evaluation and assignment are immediate

```
always @ (a or b or c)
begin
```

```
  x = a | b;           1. Evaluate  $a | b$ , assign result to x
```

```
  y = a ^ b ^ c;       2. Evaluate  $a^b^c$ , assign result to y
```

```
  z = b & ~c;          3. Evaluate  $b \& (\sim c)$ , assign result to z
```

```
end
```

- **Nonblocking assignment:** all assignments deferred until all right-hand sides have been evaluated (end of simulation timestep)

```
always @ (a or b or c)
begin
```

```
  x <= a | b;           1. Evaluate  $a | b$  but defer assignment of x
```

```
  y <= a ^ b ^ c;       2. Evaluate  $a^b^c$  but defer assignment of y
```

```
  z <= b & ~c;          3. Evaluate  $b \& (\sim c)$  but defer assignment of z
```

```
end                     4. Assign x, y, and z with their new values
```

- Sometimes, as above, both produce the same result. Sometimes, not!

Blocking and Non-blocking Assignment

```
initial
begin
  a = 1;
  b = 0;
  a = b;  // a = 0;
  b = a;  // b = 0;
end
```

```
initial
begin
  a = 1;
  b = 0;
  a <= b;  // a = 0;
  b <= a;  // b = 1;
end
```


- Blocking assignment “=”
 - Statement order matters
 - A statement has to be executed before next statement
- Non-blocking assignment “<=”
 - Concurrent assignment
 - If there are multiple non-blocking assignments to same variable in same behavior, latter overwrites previous

Blocking Assignment

- The order of statements inside an always block can affect the synthesized design
 - Verilog evaluates the assignments in an always block in the order in which they are written
 - This can cause unexpected designs

```
module example(Q1,Q2,D,Clock);  
  input D, Clock;  
  output Q1, Q2;  
  reg Q1, Q2;  
  
  always @(posedge Clock) begin  
    Q1 = D;  
    Q2 = Q1;  
  end  
endmodule
```


treated as $Q_2 = D$ since $Q_1 = D$

 

Non-blocking Assignment

- What if you wanted a “cascaded” design for the previous example?
 - The assignment to Q2 should be from the “previous” Q1
 - Need both assignments to occur in parallel on the same clock edge
 - The LHS of a non-blocking assignment is updated after all RHS values for all assignments have been evaluated
 
```
module example(Q1,Q2,D,Clock);  
  input D, Clock;  
  output Q1, Q2;  
  reg Q1, Q2;  
  
  always @(posedge Clock) begin  
    Q1 <= D;  
    Q2 <= Q1;  
  end  
endmodule
```



non-blocking assignment