


# Lecture 9

ECE 228

Mostafizur Rahman


# Function of the simple shift register

- initial state at **cycle 0**

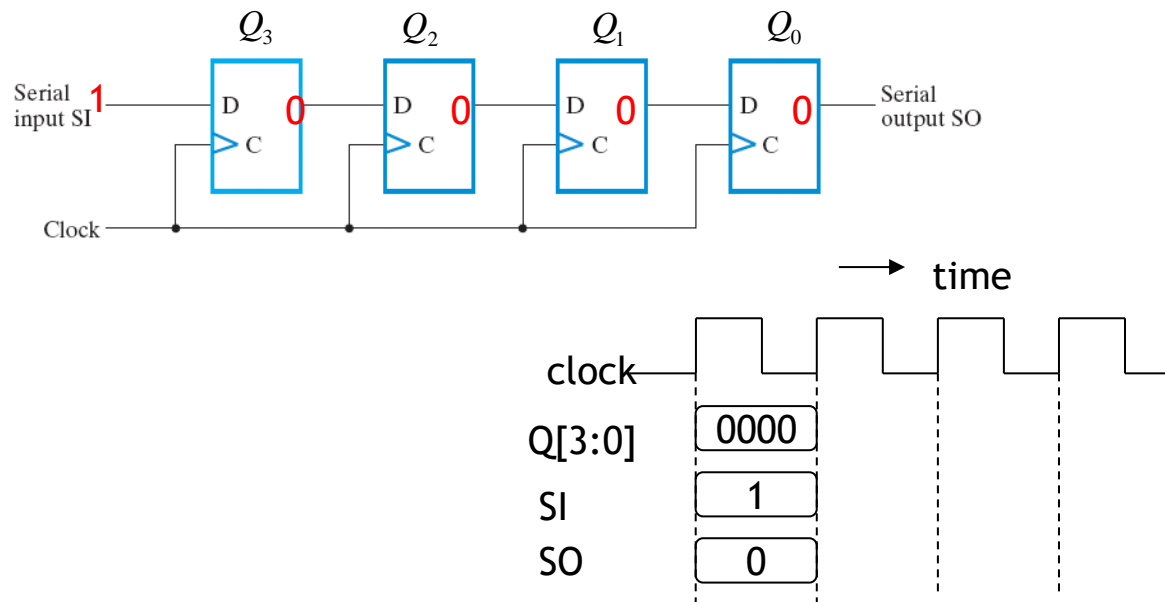


# Function of the simple shift register

- initial state at **cycle 1**

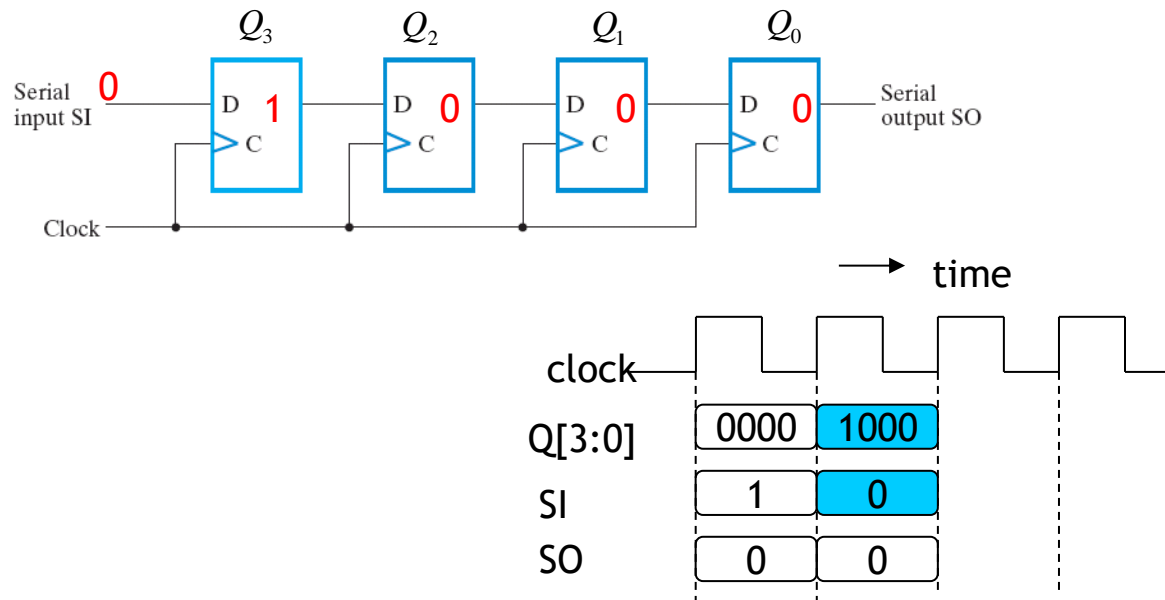

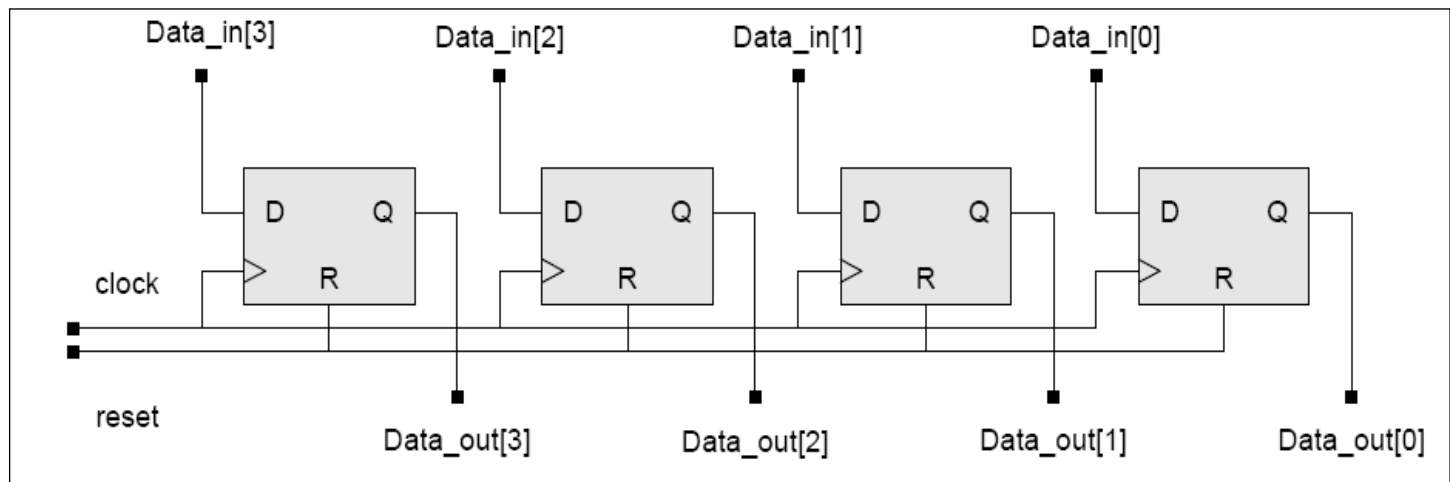
# VERILOG: Synthesis - Sequential Logic


```
module D_reg4a (Data_in, clock, reset, Data_out);  
  input [3:0] Data_in;  
  input clock, reset;  
  output [3:0] Data_out;  
  reg [3:0] Data_out;  
  always @ (posedge reset or posedge clock)  
    if (reset == 1'b1) Data_out <= 4'b0;  
    else Data_out <= Data_in;  
endmodule
```



# Timing behavior of the register

 

$$Q(t+1) = D(t)$$

 

# Activity

Write a module for 4 bit register that has `clk`, `clear`, `set` and `D` as inputs. On every clock's negative edge, the output (`Q`) gets the value `D`. If *clear* signal is ON, the register is reset to all 0s, and if *set* is ON, register is set to all 1s.

# Solution

```
module register (q,d,clk,clr_, set_) ;  
output [7:0] q ;  
input [7:0] d ;  
input clk,clr_, set_ ;  
reg [7:0] q ;  
always @ (posedge clk or negedge clr_ or negedge set_)  
    if (~clr_)  
        q = 0 ;  
    else if (~set_)  
        q = 8'b1111_1111 ;  
    else  
        q = d ;  
endmodule
```

# Sequential Circuits

- How to design custom sequential circuits?

If(X)

count = count +2

Else count = count +1




# State Machine


- We need register to hold
  - the current state
    - always @(posedge clk) block
- We need next state function
  - Where do we go from each state given the inputs
  - state by state case analysis
    - next state determined by current state and inputs
- We need the output function
  - State by state analysis
  - Moore: output determined by current state only
  - Mealy: output determined by current state and inputs

# State Machine

- Moore


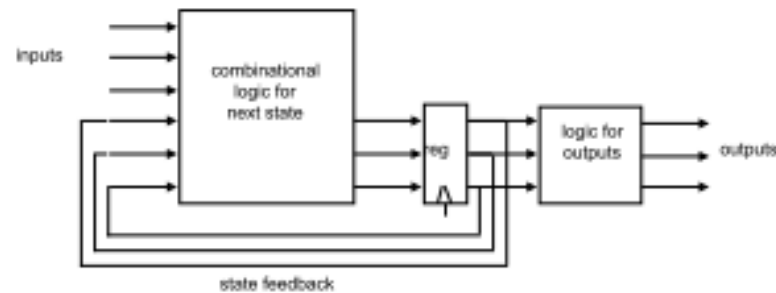


- Mealy

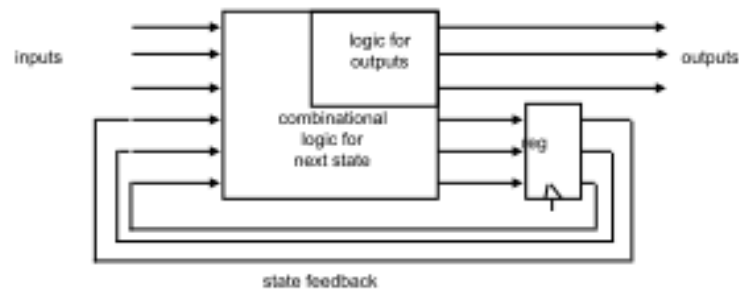
  
# Activity

- Recognize  $A, B = 0, 1$
- Mealy or Moore?



# State Register

- Declare two values
  - state : current state – output of state register
  - nxtState : next state – input to state register
  - We rely on next state function to give us nxtState
- Declare symbols for states with state assignment

```
localparam IDLE=0, WAITFORB=1,  
           DONE=2, ERROR=3;
```

```
reg [1:0] state,      // Current state  
        nxtState;    // Next state
```

# State Machine- Verilog

- Simple code for register
  - Define reset state
  - Otherwise, just move to nxtState on clock edge

```
localparam IDLE=0, WAITFORB=1,  
            DONE=2, ERROR=3;  
reg [1:0] state,    // Current state  
        nxtState; // Next state  
  
always @(posedge clk) begin  
    if (reset) begin  
        state <= IDLE;    // Initial state  
    end else begin  
        state <= nxtState;  
    end  
end
```

# State Machine-Verilog

- Combinational logic function
  - Inputs : state, inputs
  - Output : nxtState
- We could use assign statements
- We will use an **always @ (\*)** block instead
  - Allows us to use more complex statements
  - **if**
  - **case**

# State Machine-Verilog

---


- Describe what happens in each state
- Case statement is natural for this

```
always @(*) begin
    nxtState = state; // Default next state: don't move
    case (state)
        IDLE : begin
            if (B) nxtState = ERROR;
            else if (A) nxtState = WAITFORB;
        end
        WAITFORB : begin
            if (B) nxtState = DONE;
        end
        DONE : begin
        end
        ERROR : begin
        end
    endcase
end
```
 
# State Diagrams

---

- Each state is shown with a circle, labeled with the state value - the contents of the circle are the outputs
- An arc represents a transition to a different state, with the inputs indicated on the label







# Example

---

In this example, we'll be designing a controller for an elevator. The elevator can be at one of two floors: Ground or First. There is one button that controls the elevator, and it has two values: Up or Down. Also, there are two lights in the elevator that indicate the current floor: Red for Ground, and Green for First. At each time step, the controller checks the current floor and current input, changes floors and lights in the obvious way


# Example

---

  


# Example

CurrentState	Input	NextState	Red	Green
0	0	0	1	0
0	1	1	1	0
1	0	0	0	1
1	1	1	0	1

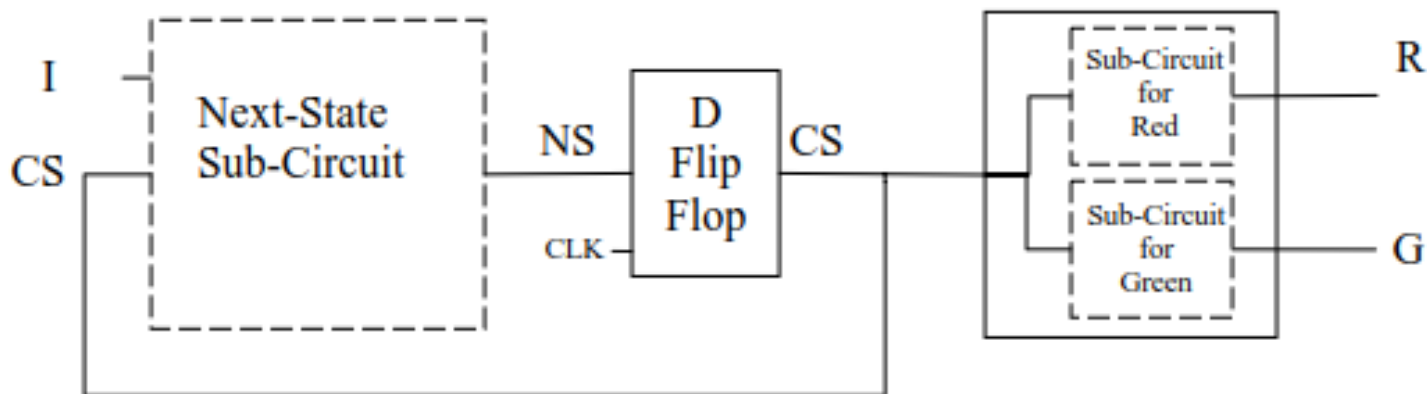


# Example

---

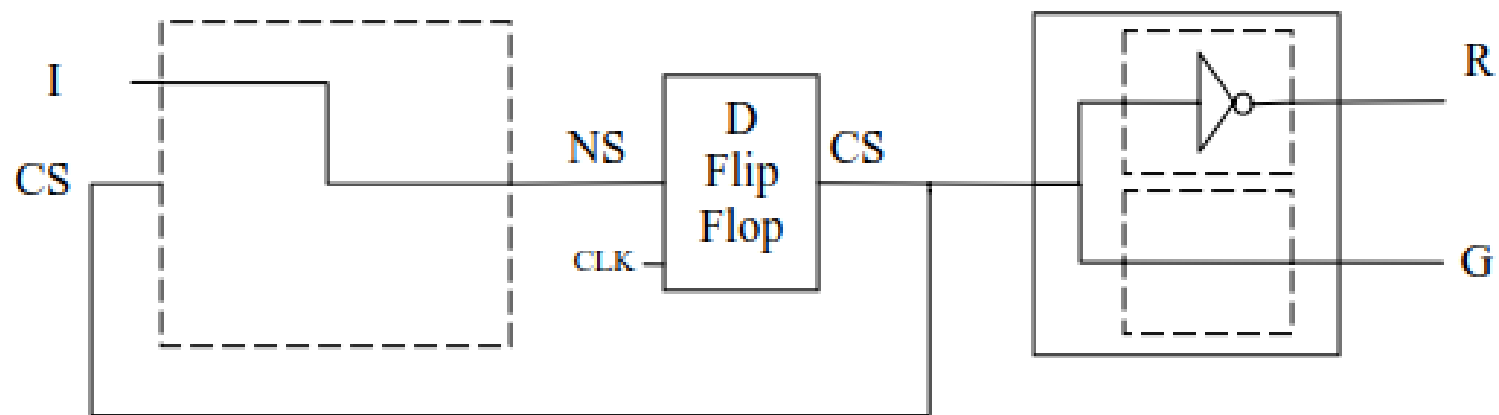


# Simple Processor's State Machine

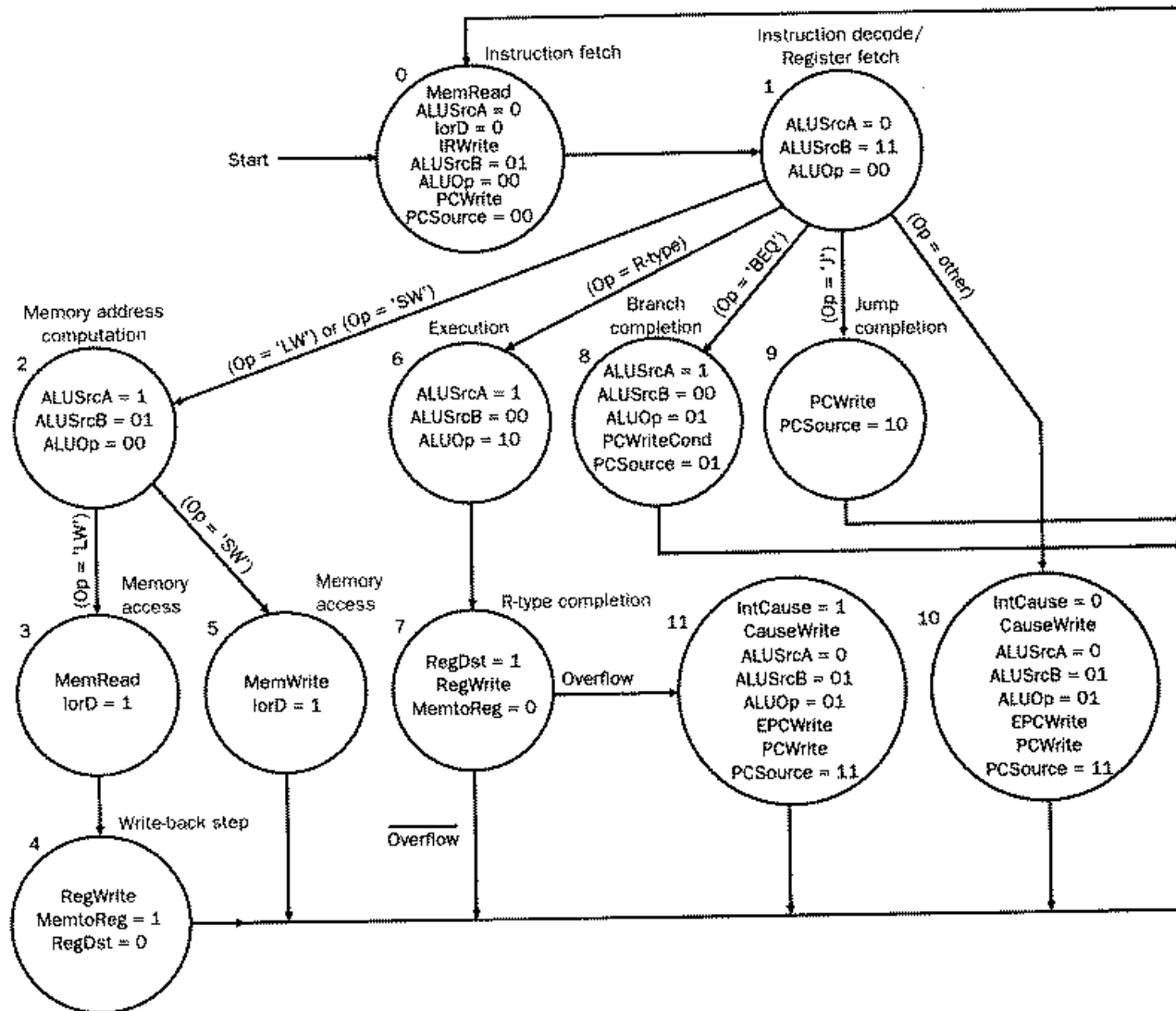

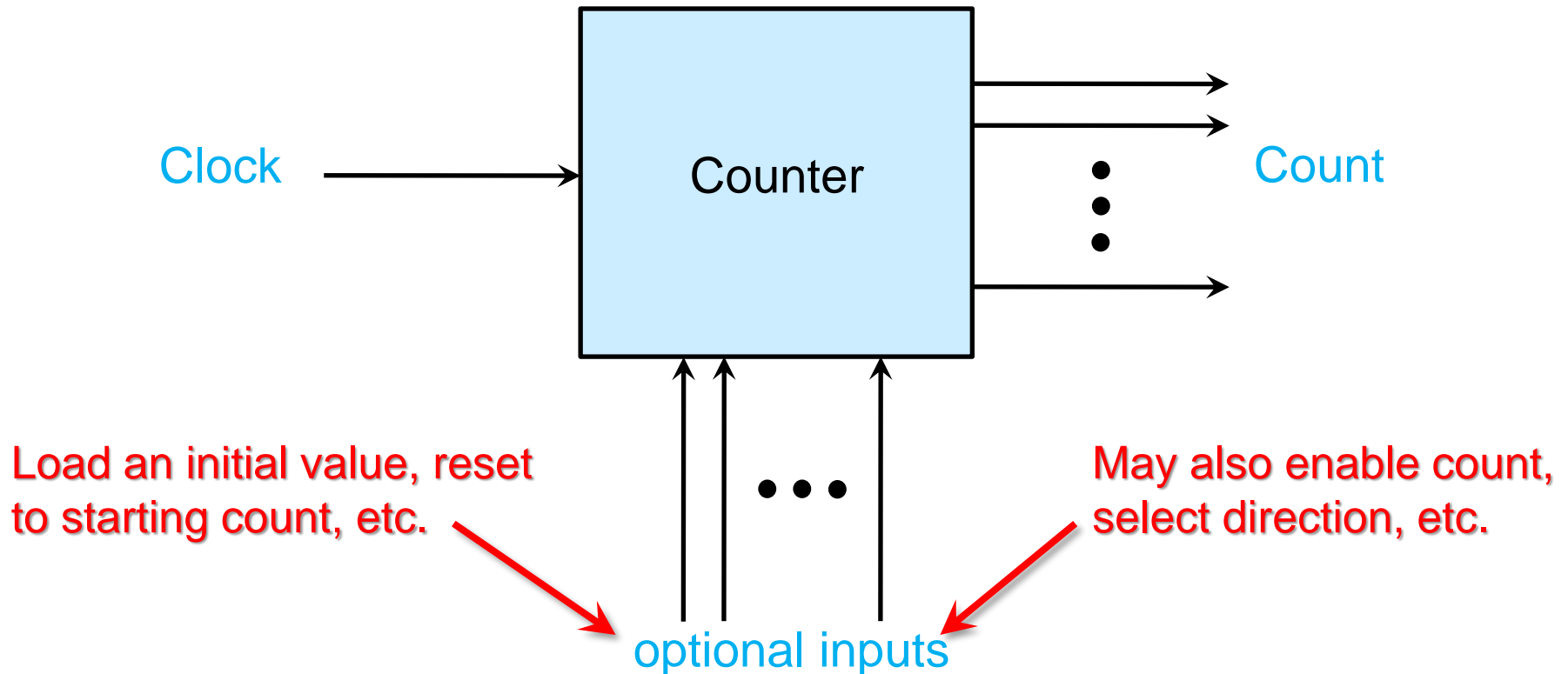
# Counters

- A counter is a circuit that produces a numeric count each time an input clock pulse makes an active transition


 
# Counter

- From another viewpoint, a counter is any sequential circuit whose state diagram is a single cycle
  - in other words, counters are a special case of a finite state machine
- Output is usually the state value, Moore machine



# Counters

---

- Counters differ by a number of basic characteristics, including:

Characteristic	Description
Modulus	Length of sequence
Coding	Count sequence
Direction	Up or down
Resettable	Reset to zero
Loadable	Load a specific value



# Two Common Types of Counters

---

- Synchronous Counters



- Clock is directly connected to the flip-flop clock inputs
- Logic is used to implement the desired state sequencing

- Asynchronous Counters


- This counter is called *asynchronous* because not all flip flops are hooked to the same clock.
- Clock connected to the flip-flop clock input on the LSB bit flip-flop
- For all other bits, a flip-flop output is connected to the clock input, thus circuit is not truly synchronous!
- slow, limited by propagation delays

# Example - Synchronous binary counter

- Function of the counter

  


# Example - Synchronous binary counter

 


$$Q(t+1) = \begin{cases} Q(t) + 1 & \text{if } EN(t) = 1 \\ Q(t) & \text{if } EN(t) = 0 \end{cases}$$
 
$$CO(t) = \begin{cases} 1 & \text{if } Q(t) = (1111)_2 \\ 0 & \text{if } Q(t) \neq (1111)_2 \end{cases}$$




# Example - Synchronous binary counter

 


$$Q(t+1) = \begin{cases} Q(t) + 1 & \text{if } EN(t) = 1 \\ Q(t) & \text{if } EN(t) = 0 \end{cases}$$
 
$$CO(t) = \begin{cases} 1 & \text{if } Q(t) = (1111)_2 \\ 0 & \text{if } Q(t) \neq (1111)_2 \end{cases}$$




# Example - Synchronous binary counter

 


$$Q(t+1) = \begin{cases} Q(t) + 1 & \text{if } EN(t) = 1 \\ Q(t) & \text{if } EN(t) = 0 \end{cases}$$
 
$$CO(t) = \begin{cases} 1 & \text{if } Q(t) = (1111)_2 \\ 0 & \text{if } Q(t) \neq (1111)_2 \end{cases}$$




# Example - Synchronous binary counter

 


$$Q(t+1) = \begin{cases} Q(t) + 1 & \text{if } EN(t) = 1 \\ Q(t) & \text{if } EN(t) = 0 \end{cases}$$
 
$$CO(t) = \begin{cases} 1 & \text{if } Q(t) = (1111)_2 \\ 0 & \text{if } Q(t) \neq (1111)_2 \end{cases}$$




# Example - Synchronous binary counter

 


$$Q(t+1) = \begin{cases} Q(t) + 1 & \text{if } EN(t) = 1 \\ Q(t) & \text{if } EN(t) = 0 \end{cases}$$
 
$$CO(t) = \begin{cases} 1 & \text{if } Q(t) = (1111)_2 \\ 0 & \text{if } Q(t) \neq (1111)_2 \end{cases}$$




# Example - Synchronous binary counter

 


$$Q(t+1) = \begin{cases} Q(t) + 1 & \text{if } EN(t) = 1 \\ Q(t) & \text{if } EN(t) = 0 \end{cases}$$
 
$$CO(t) = \begin{cases} 1 & \text{if } Q(t) = (1111)_2 \\ 0 & \text{if } Q(t) \neq (1111)_2 \end{cases}$$






# The Spec

 


$$Q(t+1) = \begin{cases} Q(t) + 1 & \text{if } EN(t) = 1 \\ Q(t) & \text{if } EN(t) = 0 \end{cases}$$
 
$$CO(t) = \begin{cases} 1 & \text{if } Q(t) = (1111)_2 \\ 0 & \text{if } Q(t) \neq (1111)_2 \end{cases}$$




# Example - Synchronous binary counter

 


$$Q(t+1) = \begin{cases} Q(t) + 1 & \text{if } EN(t) = 1 \\ Q(t) & \text{if } EN(t) = 0 \end{cases}$$
 
$$CO(t) = \begin{cases} 1 & \text{if } Q(t) = (1111)_2 \\ 0 & \text{if } Q(t) \neq (1111)_2 \end{cases}$$


 
# Modulus Counters


- Modulus
  - number of states in a counter's cycle
- Given  $m$  states
  - modulo- $m$  counter or divide-by- $m$  counter
  - Count is remainder of division by  $m$ ;  $m$  may not be a power of 2
- Power-of-2 counters use all states
- Non-power-of-2 counters have extra, unused states



- Example: 4-bit Binary / Hex / Mod-16 Counter  
0000, 0001, 0010, ... 1110, 1111, 0000, 0001, ...
  - All states used
- 4-bit BCD / Decade / Mod-10 Counter  
0000, 0001, 0010, ... 1000, 1001, 0000, 0001, ...
  - 6 unused states

 
## More complex counters

- An example of full-featured 4-Bit Synchronous counter:
  - It can increment or decrement, by setting the **UP** input to 1 or 0.
  - You can immediately (asynchronously) clear the counter to 0000 by setting **CLR** = 1.
  - You can specify the counter's next output by setting **D<sub>3</sub>-D<sub>0</sub>** to any four-bit value and clearing **LD**.
  - The active-low **EN** input enables or disables the counter.
    - When the counter is disabled, it continues to output the same value without incrementing, decrementing, loading, or clearing.
  - The “counter out” **CO** is normally 1, but becomes 0 when the counter reaches its maximum value, 1111.



 
# An 8-bit counter

- As you might expect by now, we can use these general counters to build other counters.
- Here is an 8-bit counter made from two 4-bit counters.
  - The bottom counter represents the least significant four bits, while the top counter represents the most significant four bits.
  - When the bottom counter reaches 1111 (i.e., when  $CO = 0$ ), it enables the top counter for one cycle.
  - The counters share clock and clear signals.



 
## A restricted 4-bit counter

- We can also make a counter that “starts” at some value besides 0000.
- In the diagram below, when CO=0 the LD signal forces the next state to be loaded from D<sub>3</sub>-D<sub>0</sub>.
- The result is this counter wraps from 1111 to 0110 (instead of 0000).



 
## Another restricted counter

- We can also make a circuit that counts up to only 1100, instead of 1111.
- Here, when the counter value reaches 1100, the NAND gate forces the counter to load, so the next state becomes 0000.



# 3-bit Verilog Up/Down Counter w/ parallel load

---

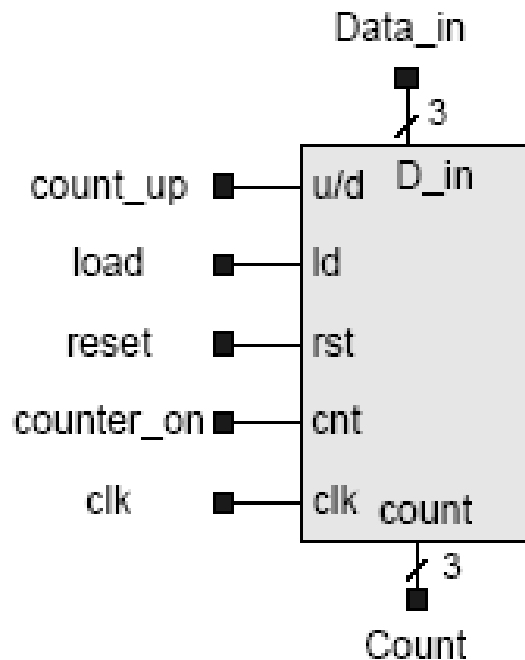


## Functional Specs.

- Load counter with `Data_in` when `load = 1`
- Counter counts when `counter_on = 1`
  - counts-up when `count_up = 1`
  - Counts-down when `count_up = 0`



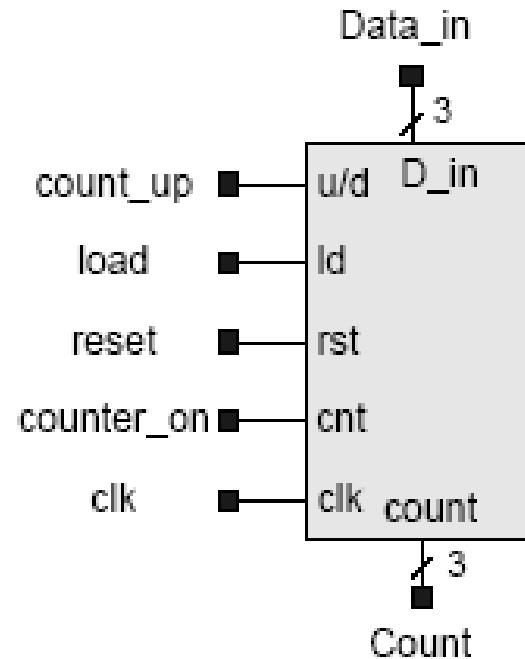
## Verilog Up/Down Counter (cont.)

```
module up_down_counter (clk, reset, load, count_up, counter_on, Data_in, Count);  
  input clk, reset, load, count_up, counter_on;  
  input [2:0] Data_in;  
  output [2:0] Count;  
  reg [2:0] Count;  
  
  always @ (posedge reset or posedge clk)  
    if (reset == 1'b1)  
      Count = 3'b0;  
    else if (load == 1'b1)  
      Count = Data_in;  
    else if (counter_on == 1'b1) begin  
      if (count_up == 1'b1)  
        Count = Count + 1;  
      else Count = Count - 1;  
    end  
endmodule
```



# Verilog 4-bit Ripple Counter

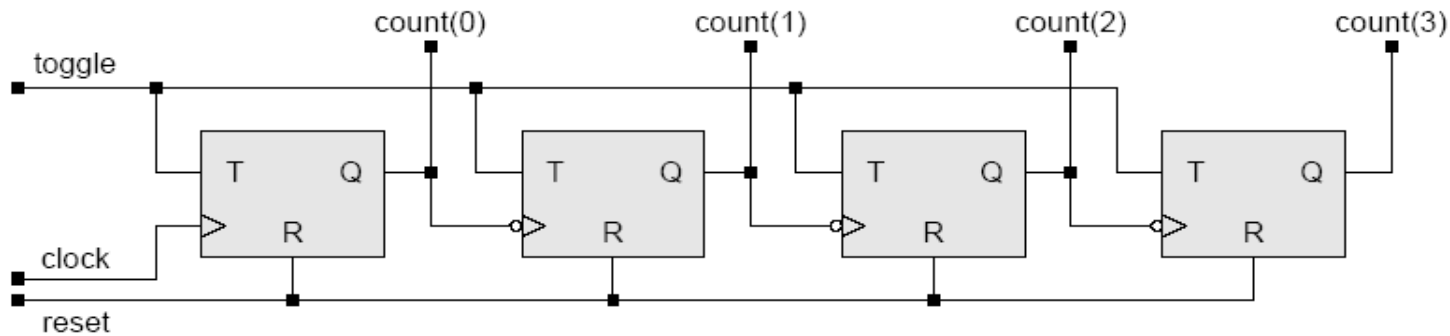


```
module ripple_counter (clock, toggle, reset, count);  
  input clock, toggle, reset;  
  output [3:0] count;  
  reg [3:0] count;  
  wire c0, c1, c2;  
  assign c0 = count[0], c1 = count[1], c2 = count[2];  
  
  always @ (posedge reset or posedge clock)  
    if (reset == 1'b1) count[0] <= 1'b0;  
    else if (toggle == 1'b1) count[0] <= ~count[0];  
  
  always @ (posedge reset or negedge c0)  
    if (reset == 1'b1) count[1] <= 1'b0;  
    else if (toggle == 1'b1) count[1] <= ~count[1];  
  
  always @ (posedge reset or negedge c1)  
    if (reset == 1'b1) count[2] <= 1'b0;  
    else if (toggle == 1'b1) count[2] <= ~count[2];  
  
  always @ (posedge reset or negedge c2)  
    if (reset == 1'b1) count[3] <= 1'b0;  
    else if (toggle == 1'b1) count[3] <= ~count[3];  
endmodule
```

 
# Digital clock

---


- refresh the time every one second
- 00:59 -> 01:00




# Architecture

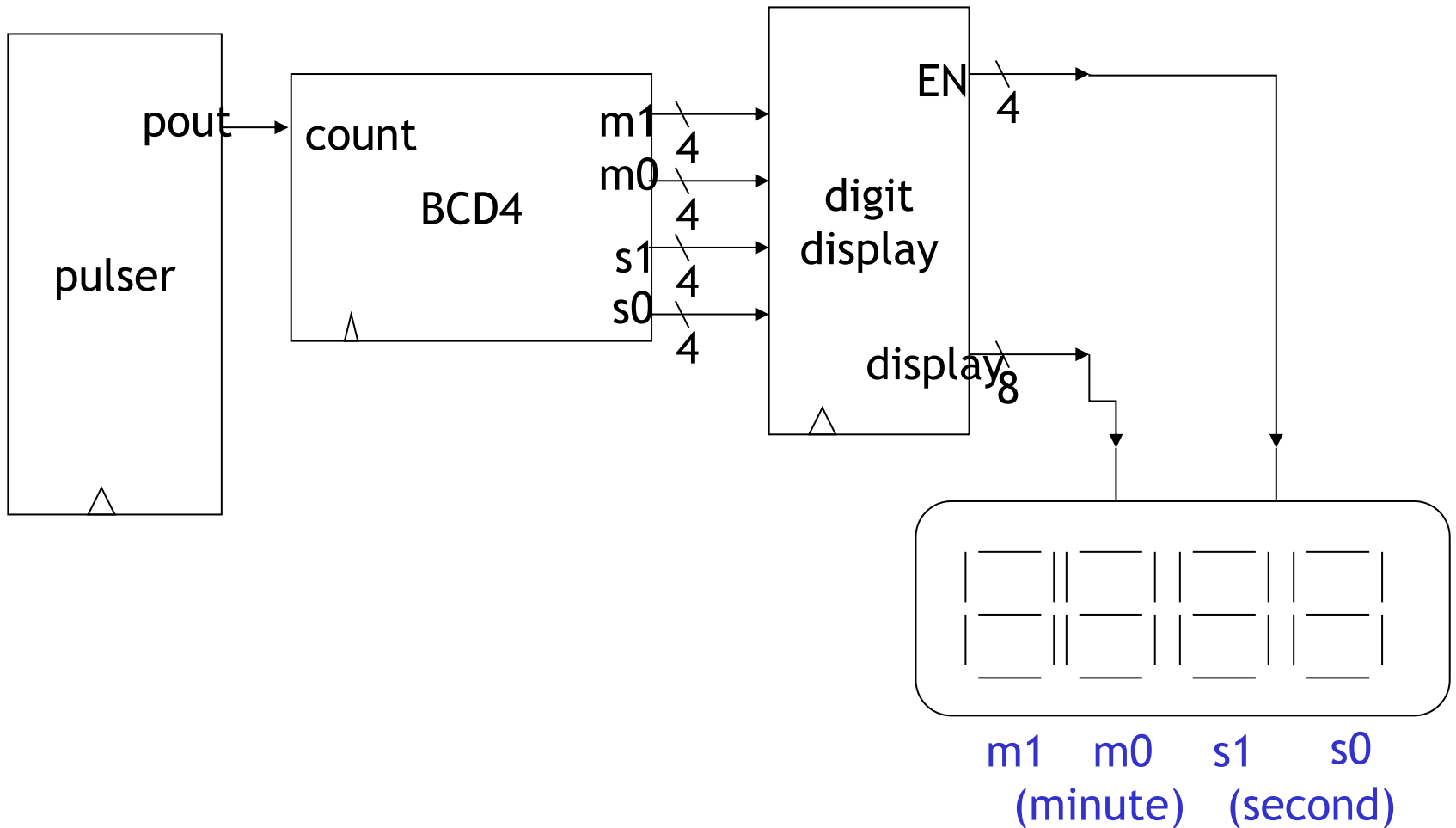

# Architecture

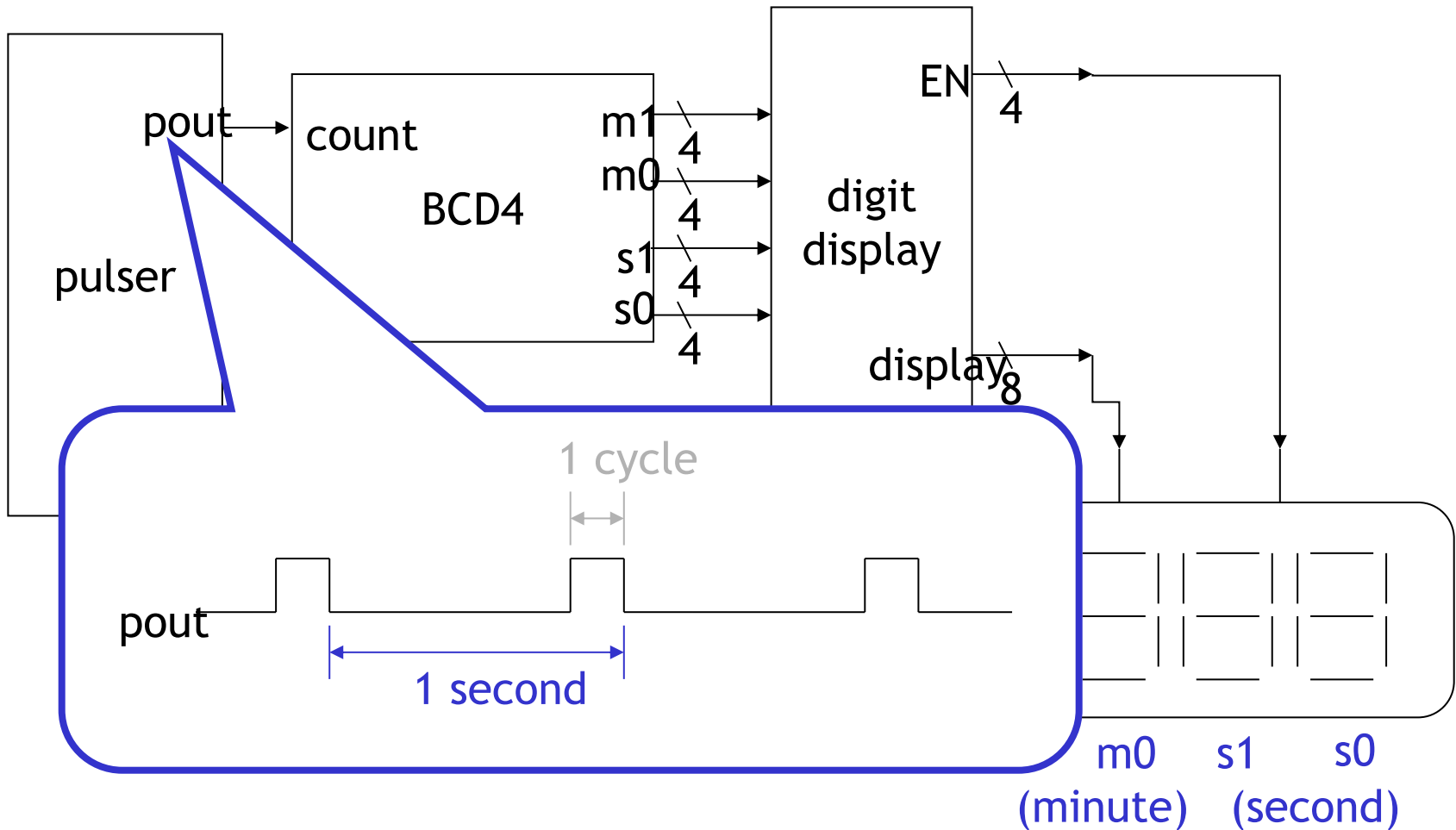


# Architecture

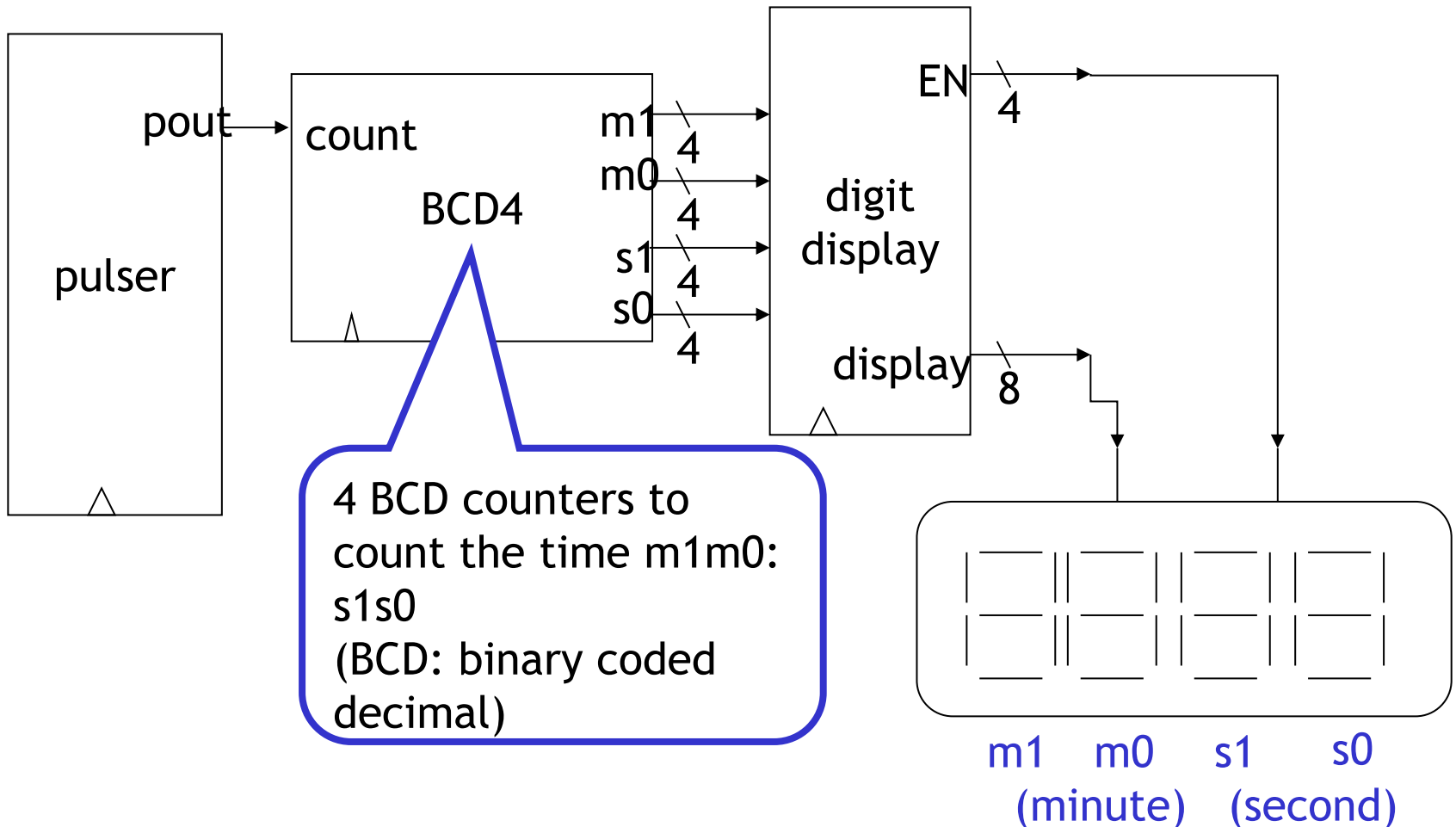


# The pulser

---

 
 
# Design the pulser


- up-counter within the pulser
- send out a pulse when counter==999






# Pulser design

---

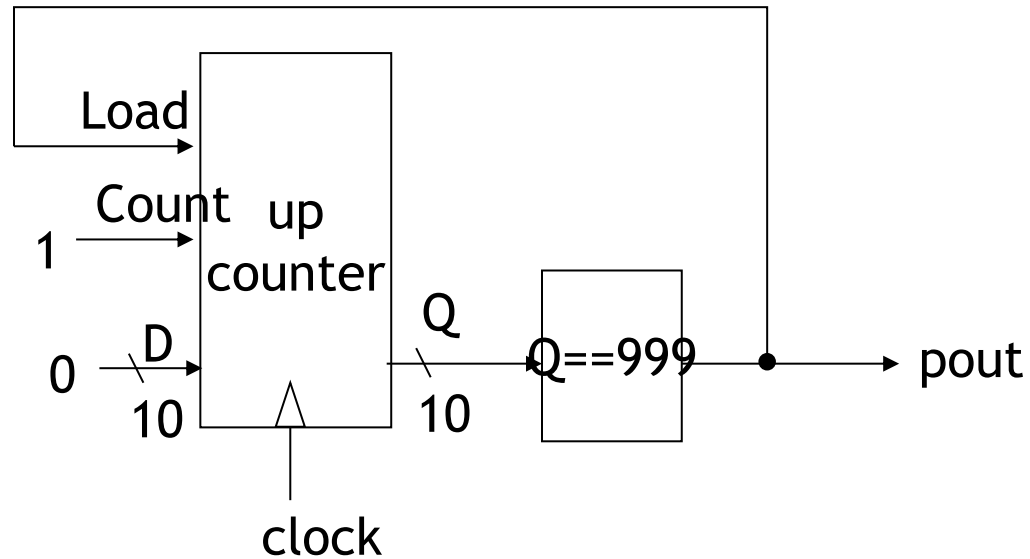


# How the pulser works

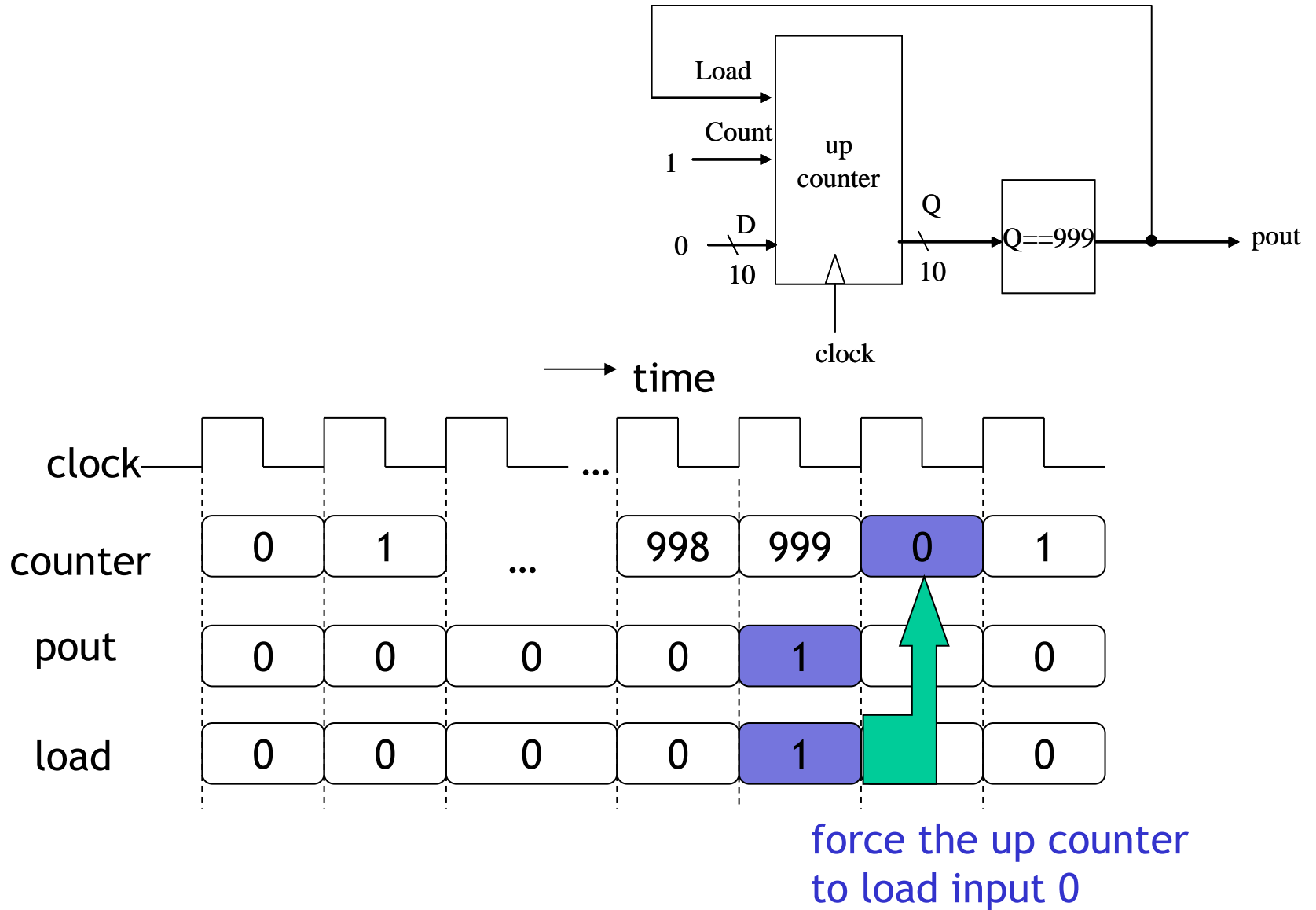


# How to check equal?

---


- $\text{pout}=1$  iff  $Q=999$ ?

 


# General scheme to check $A==B$ ?

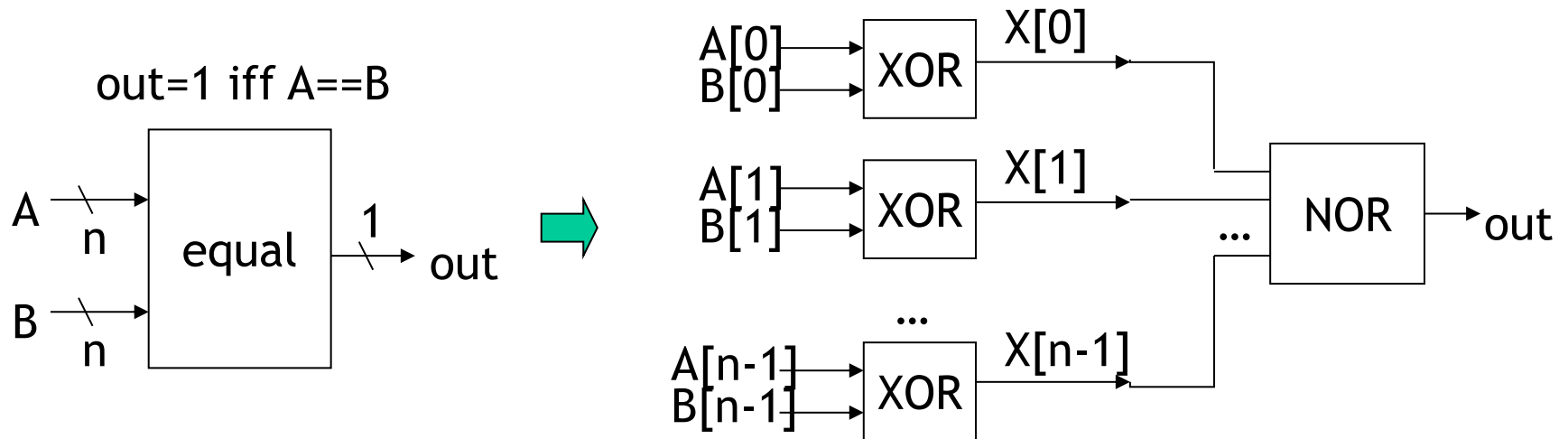

# The counter architecture for m1m0:s1s0

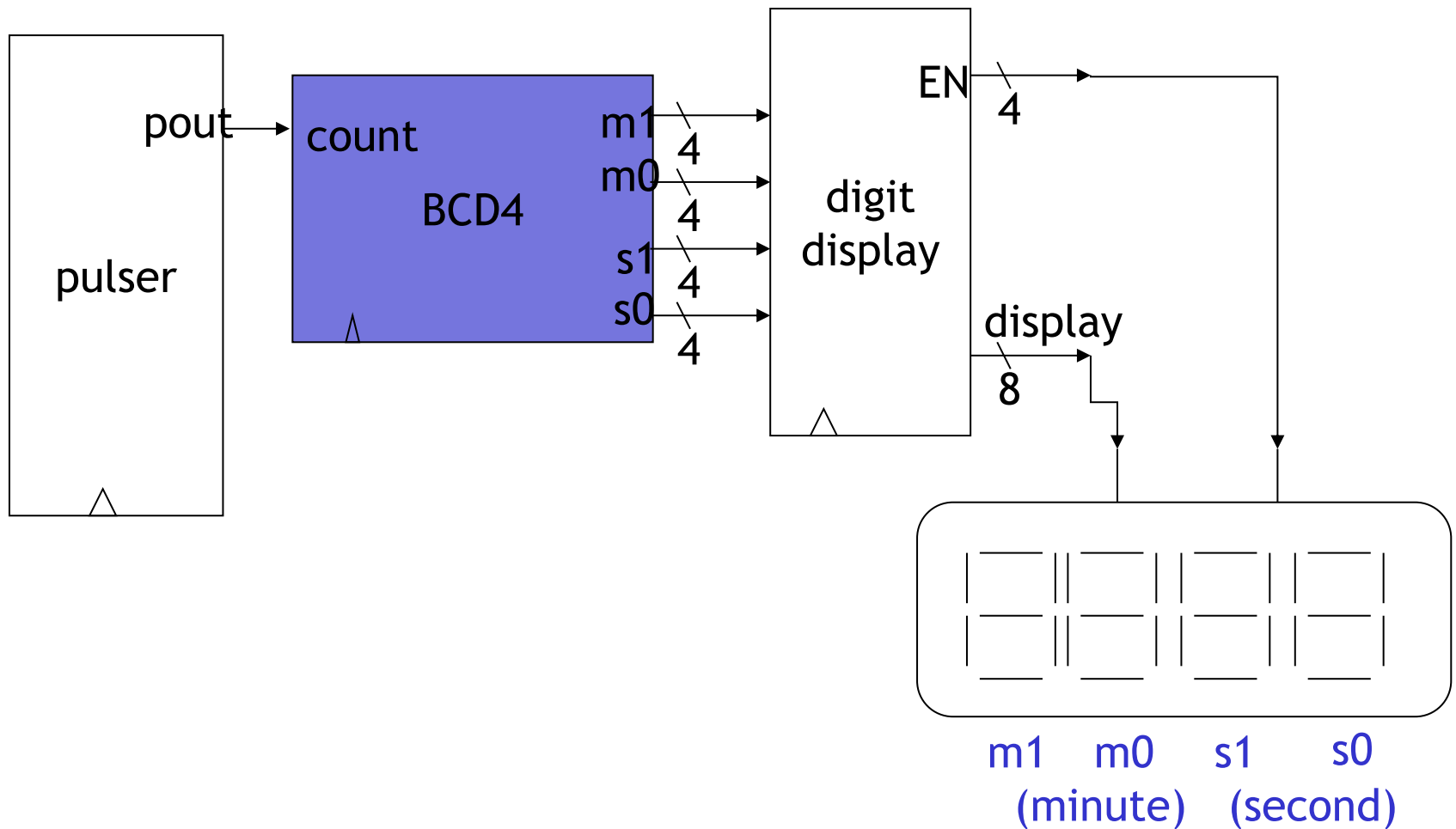


# Architecture of the counter

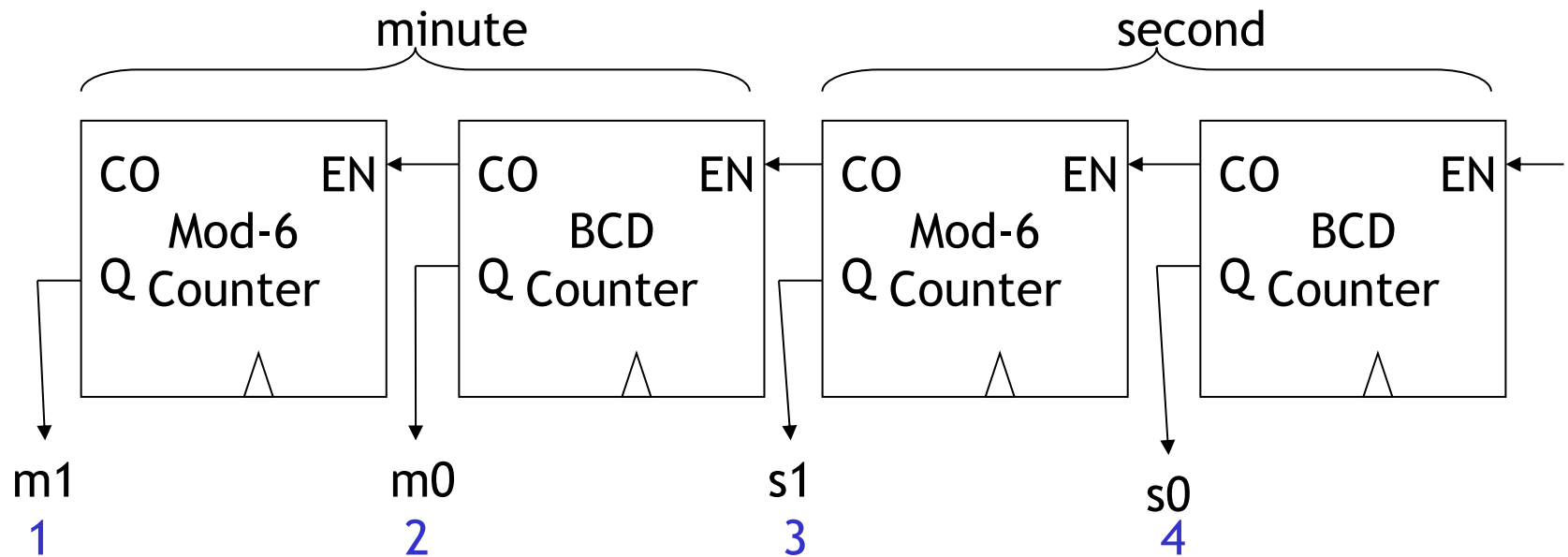


current time: 12:34

# Architecture of the counter

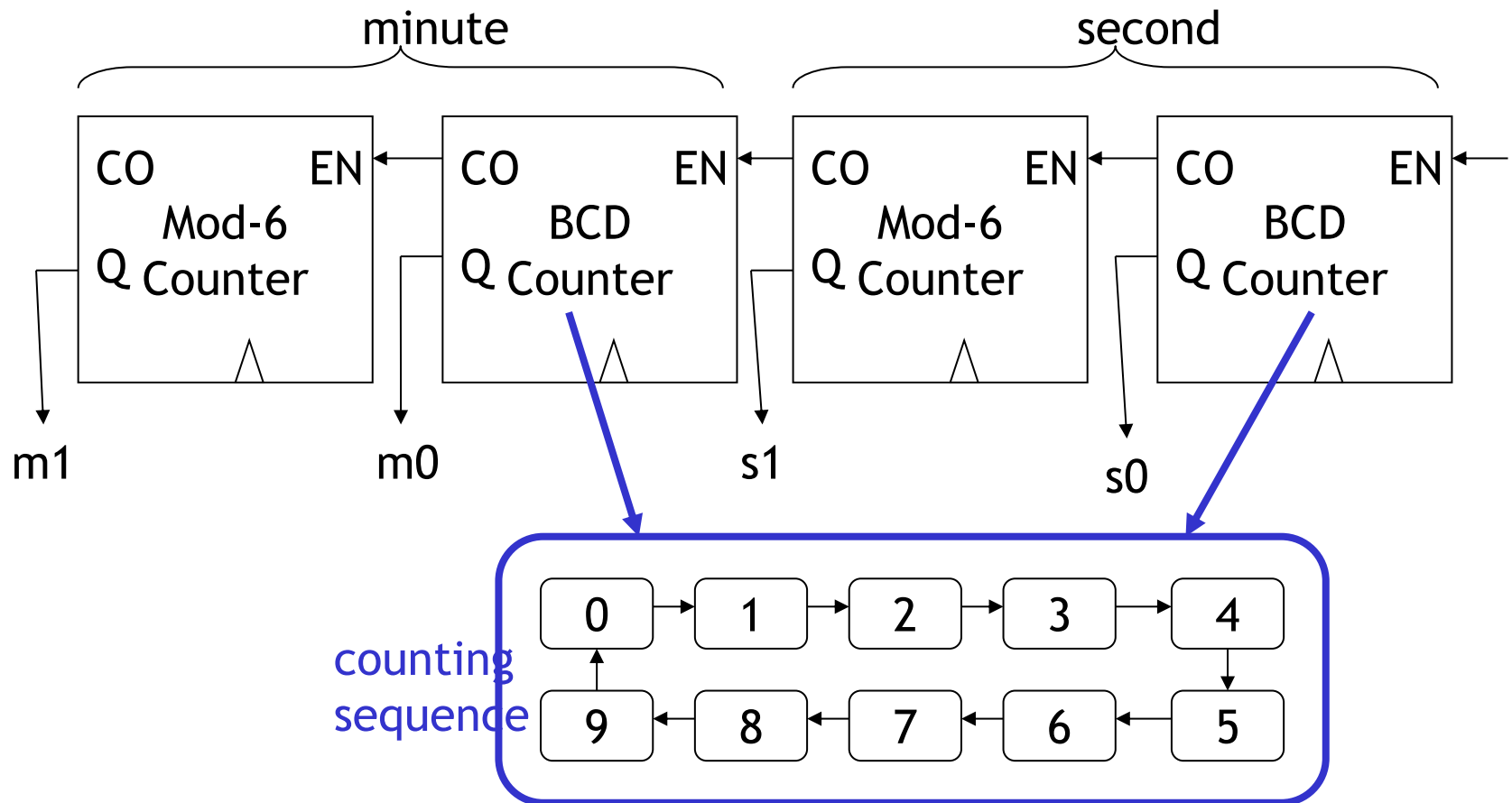


# Architecture of the counter

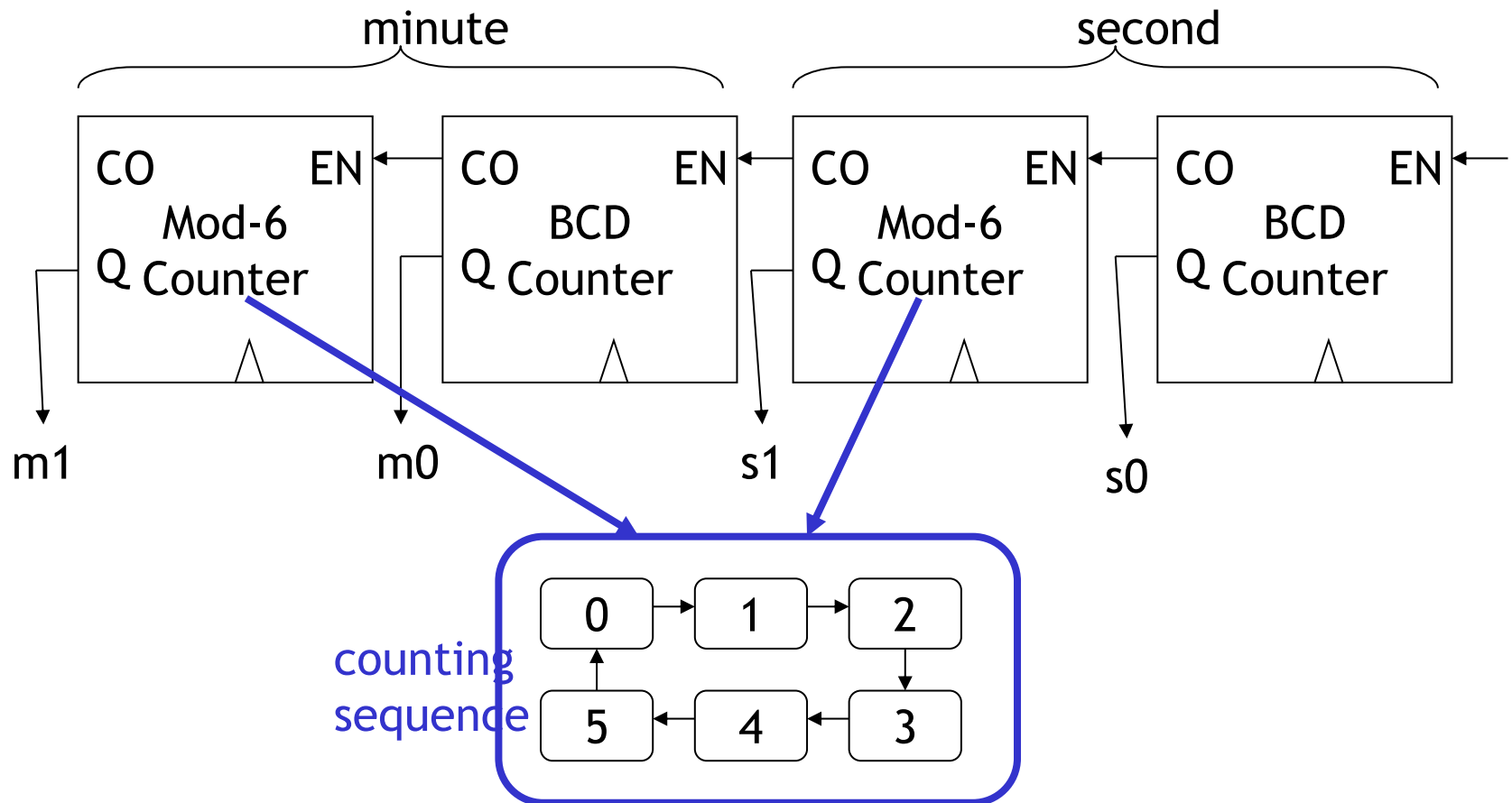



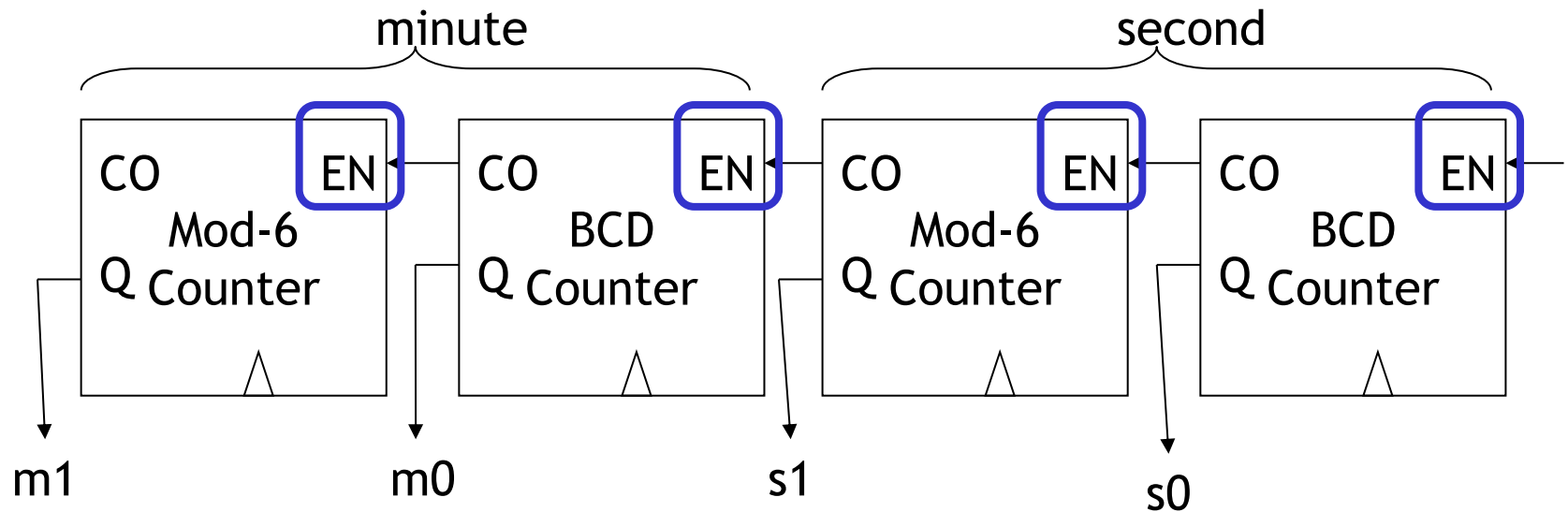
# Architecture of the counter

- each counter receives an enable signal to make  $Q(t+1)=Q(t)+1$
- the counting is triggered by previous digit or pulser



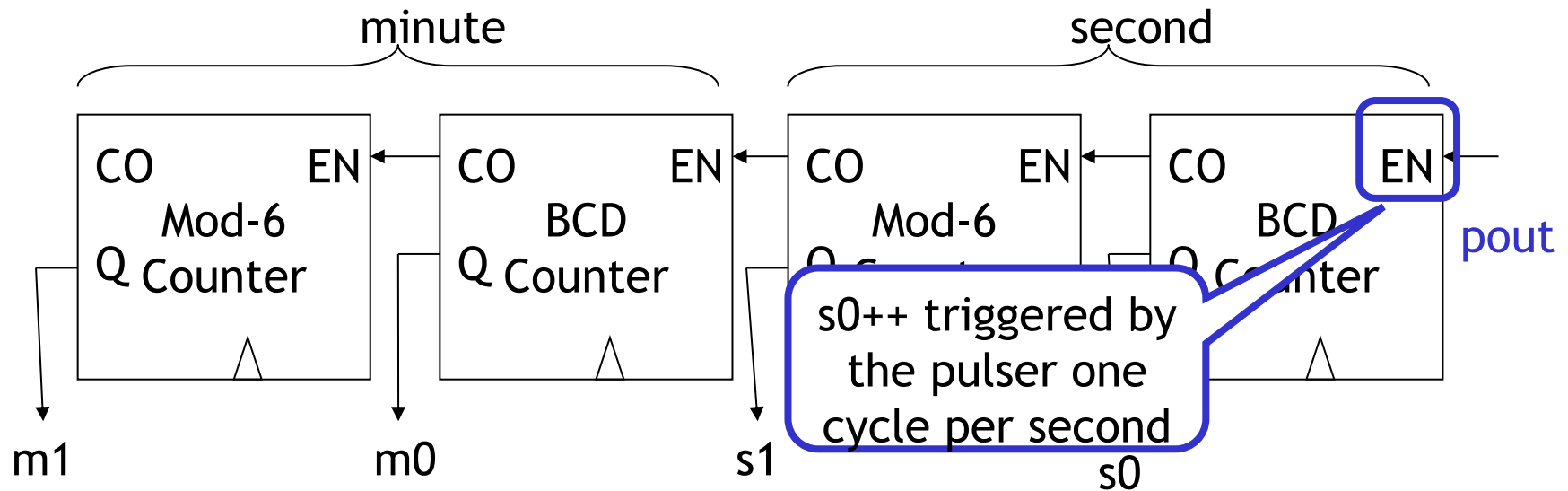
# Architecture of the counter

- each counter receives an enable signal to make  $Q(t+1)=Q(t)+1$
- the counting is triggered by previous digit or pulser




# Timing diagram of carry-in

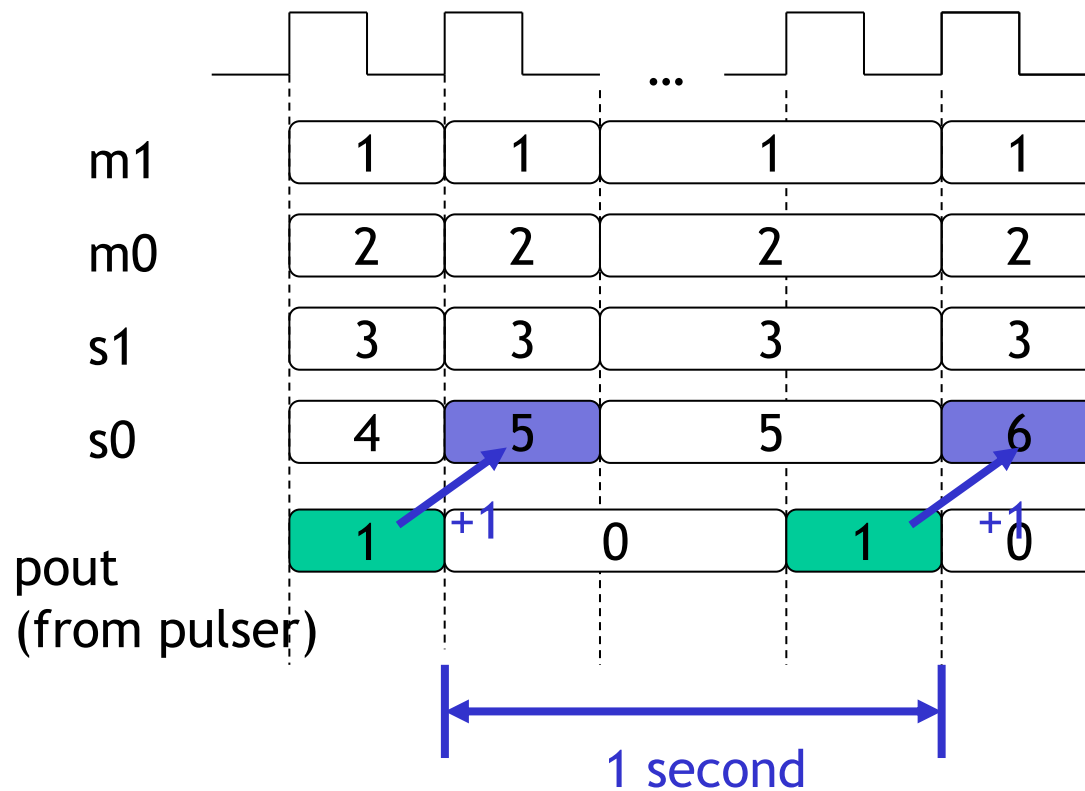

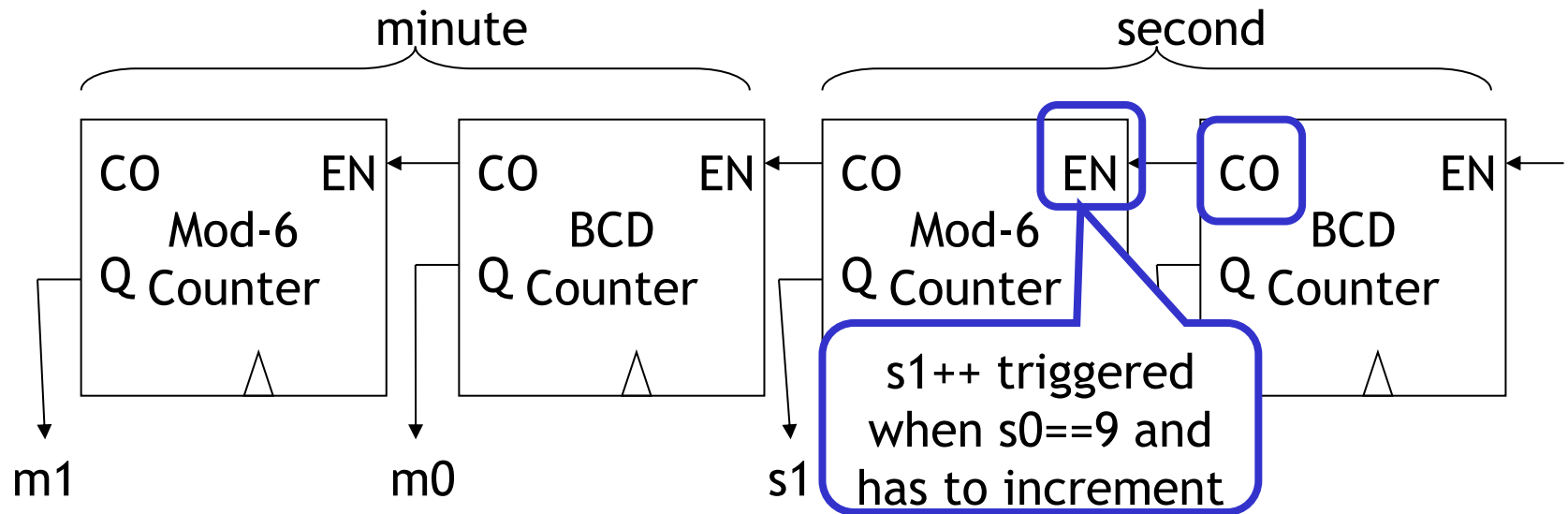
# Architecture of the counter

- each counter receives an enable signal to make  $Q(t+1)=Q(t)+1$
- the counting is triggered by previous digit or pulser




# Timing diagram of carry-in

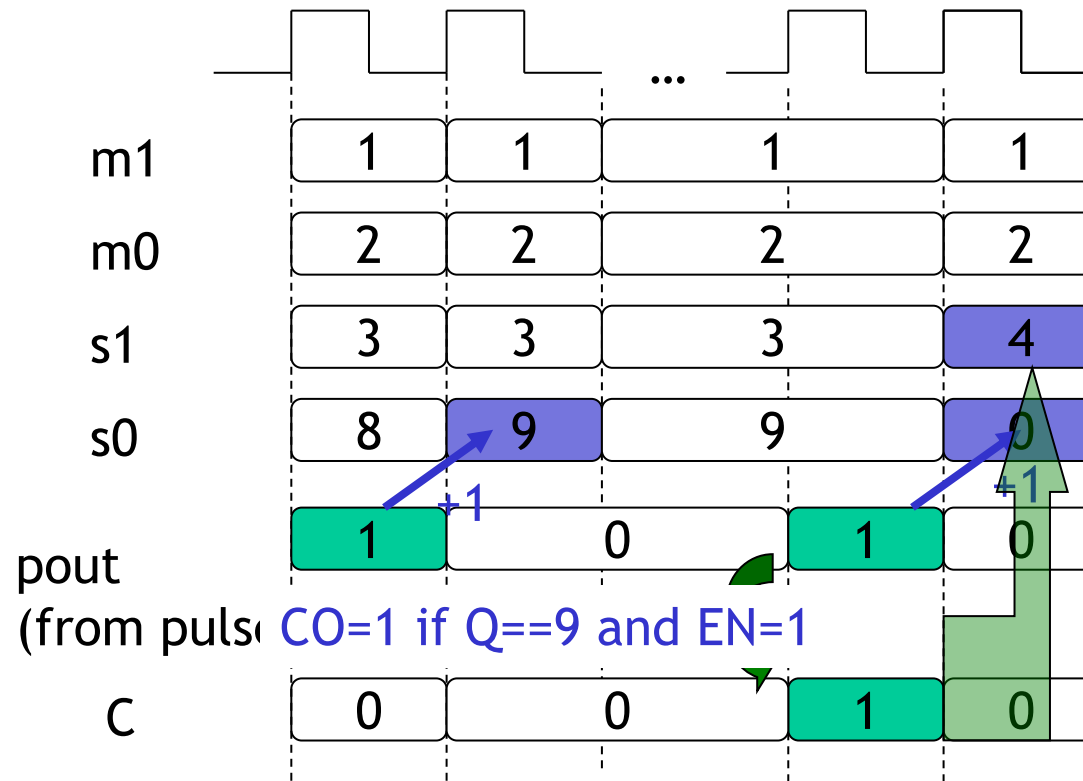

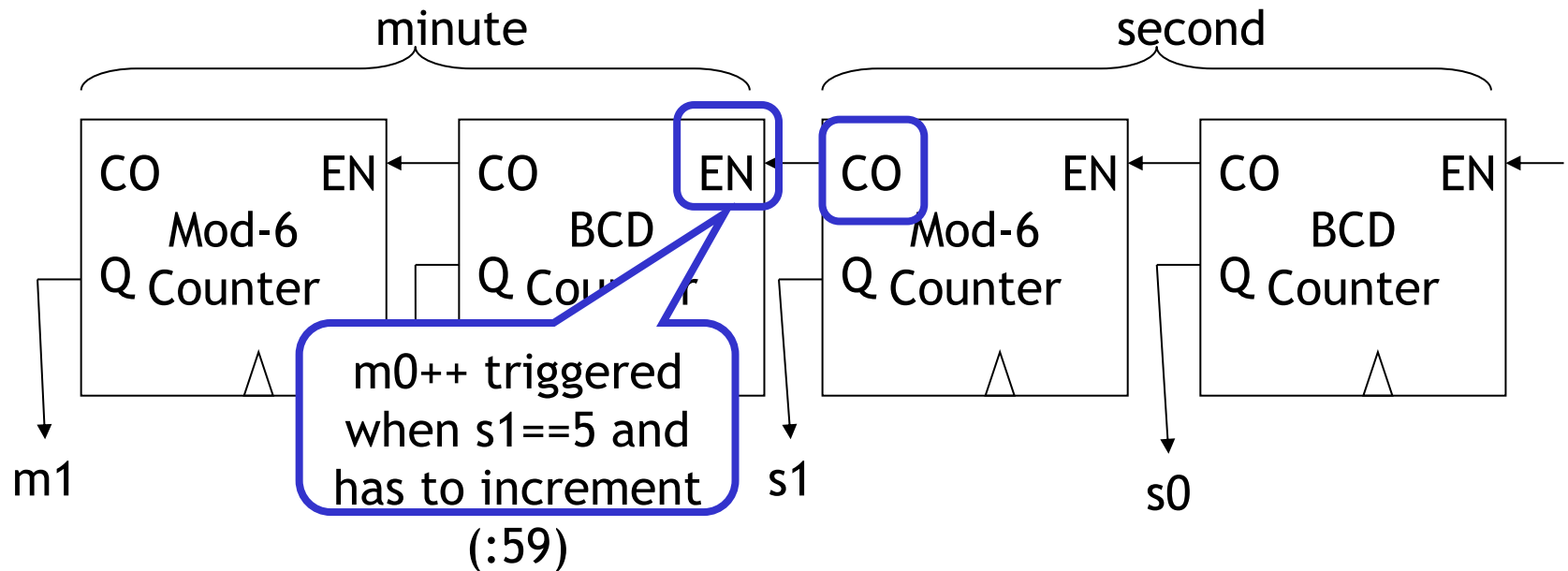
# Architecture of the counter


- each counter receives an enable signal to make  $Q(t+1)=Q(t)+1$
- the counting is triggered by previous digit or pulser



# 7-Segment Digit Display Architecture

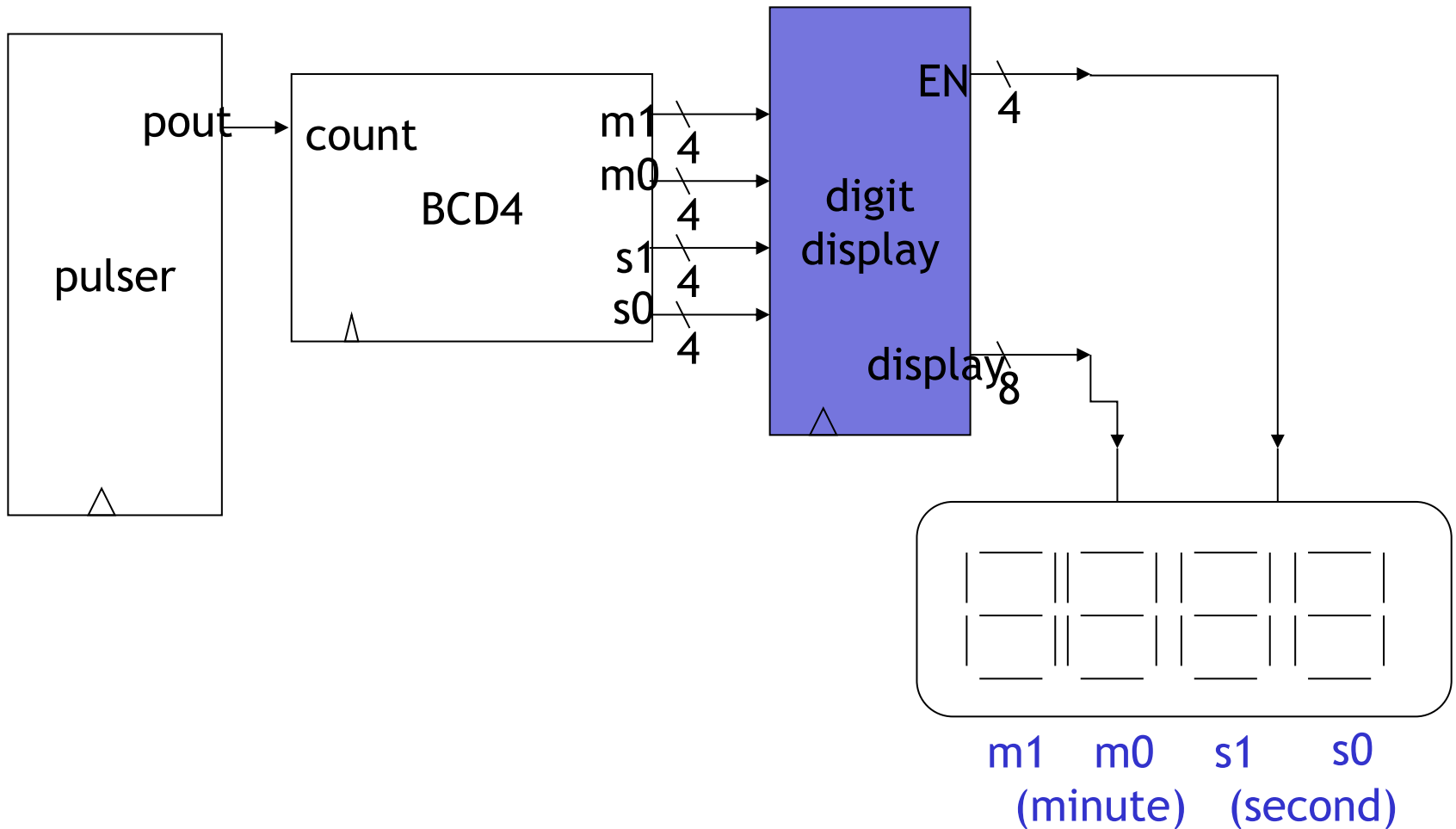

# 7-segment LED display

 




# Group of 7-seg digit display


---

- sharing decoded display signal

 


# Group of 7-seg digit display

- sharing decoded display signal

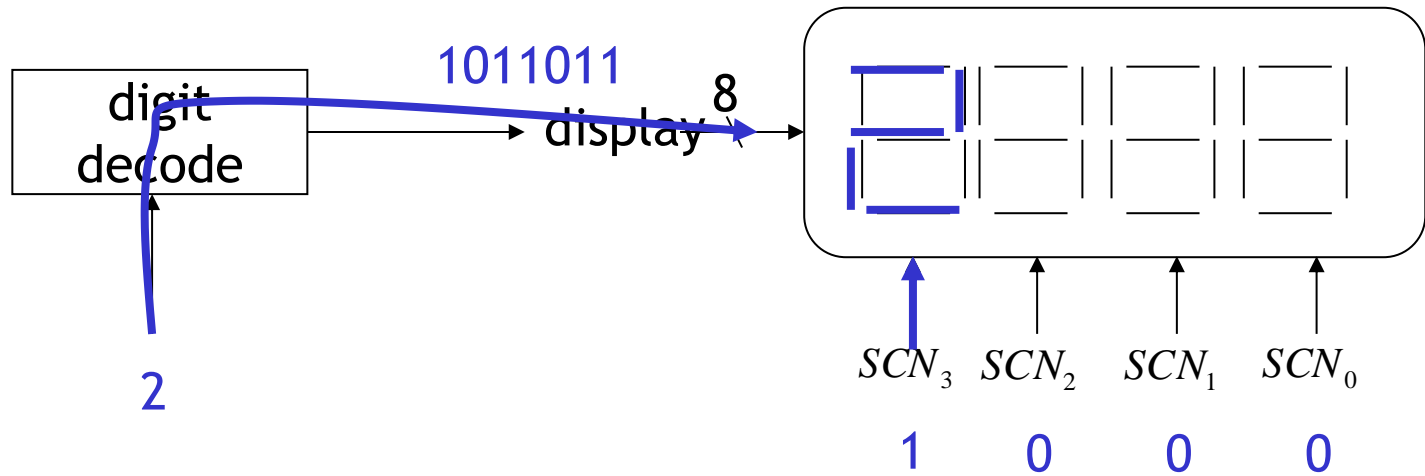


# Group of 7-seg digit display

- sharing decoded display signal

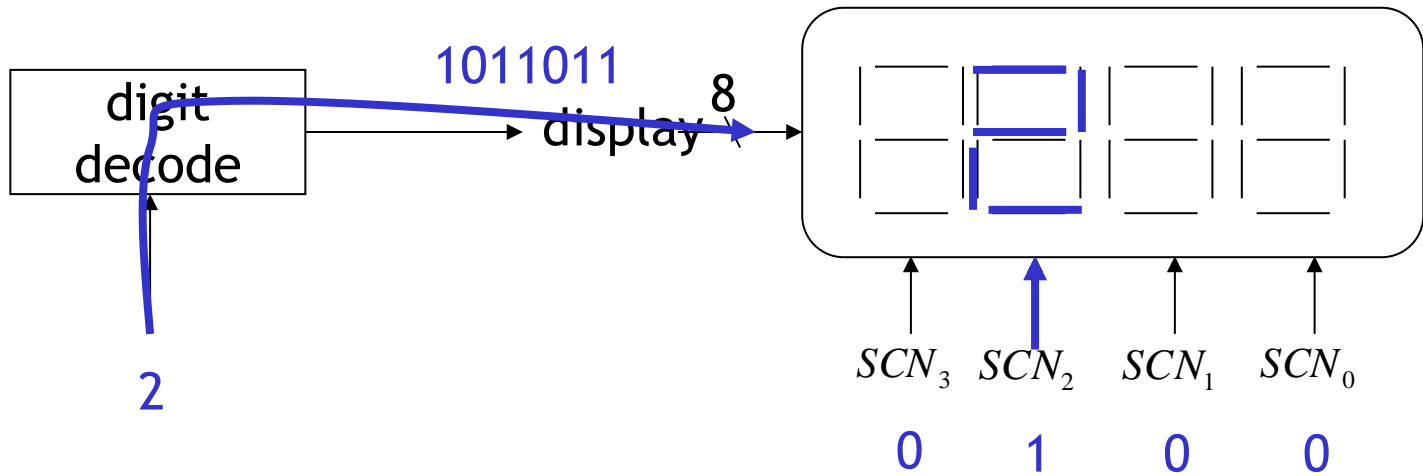


# Group of 7-seg digit display

- sharing decoded display signal

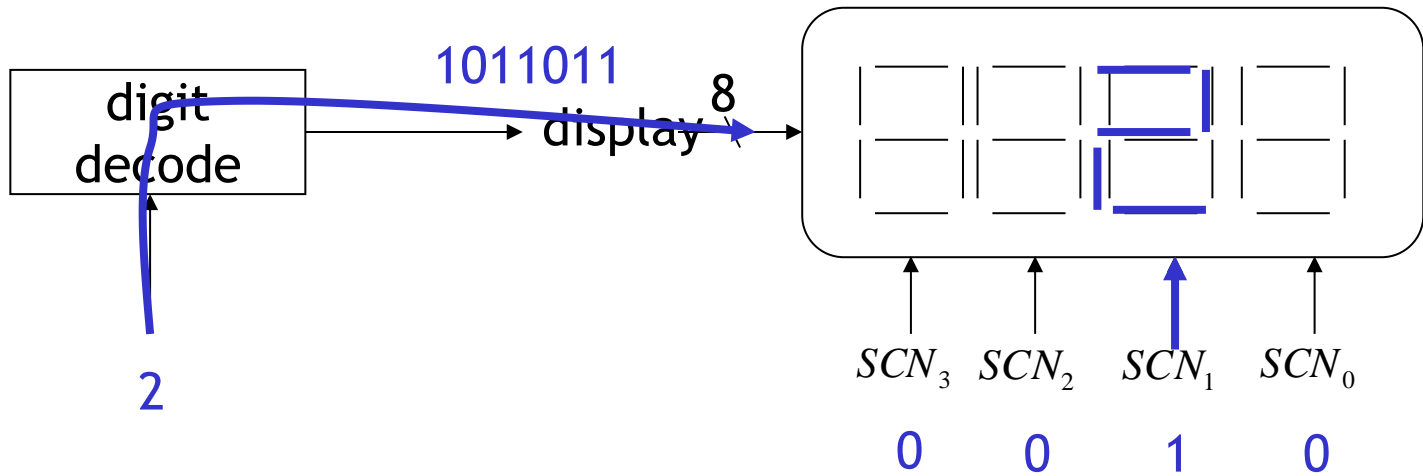


# Group of 7-seg digit display


- sharing decoded display signal

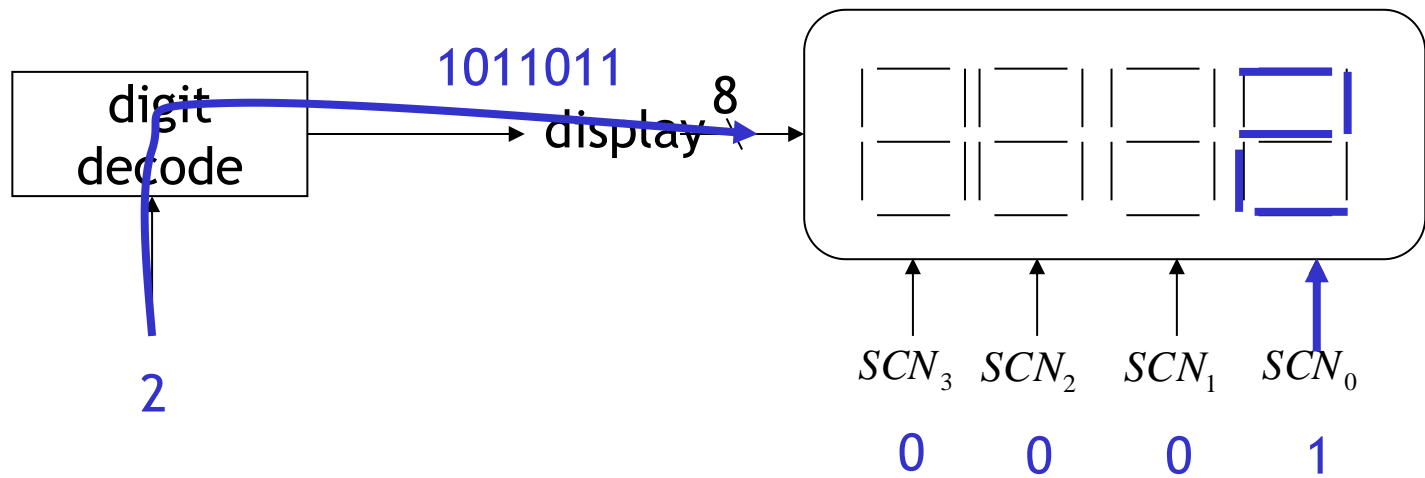


# General Design Diagram

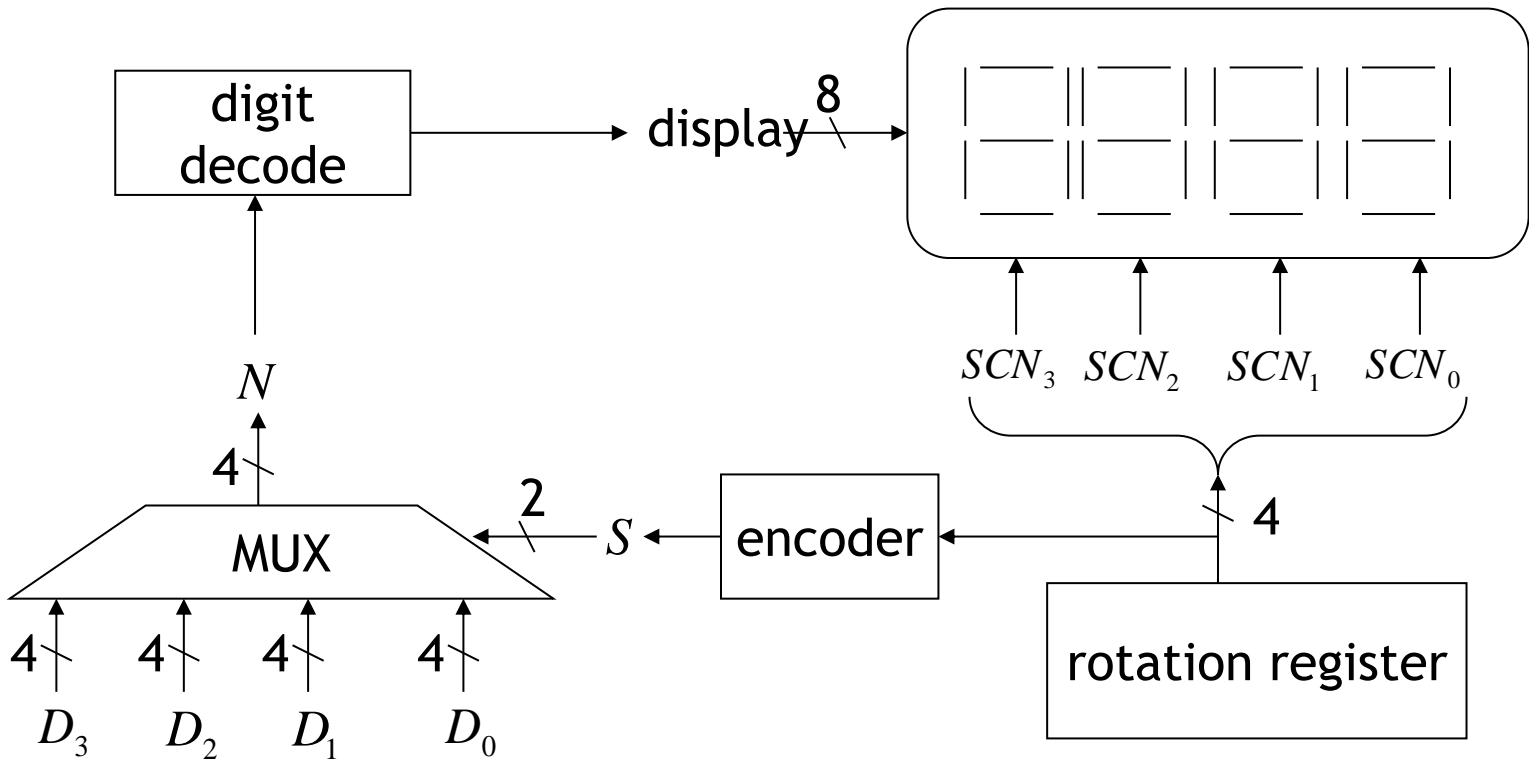

# Rotation register to send SCN

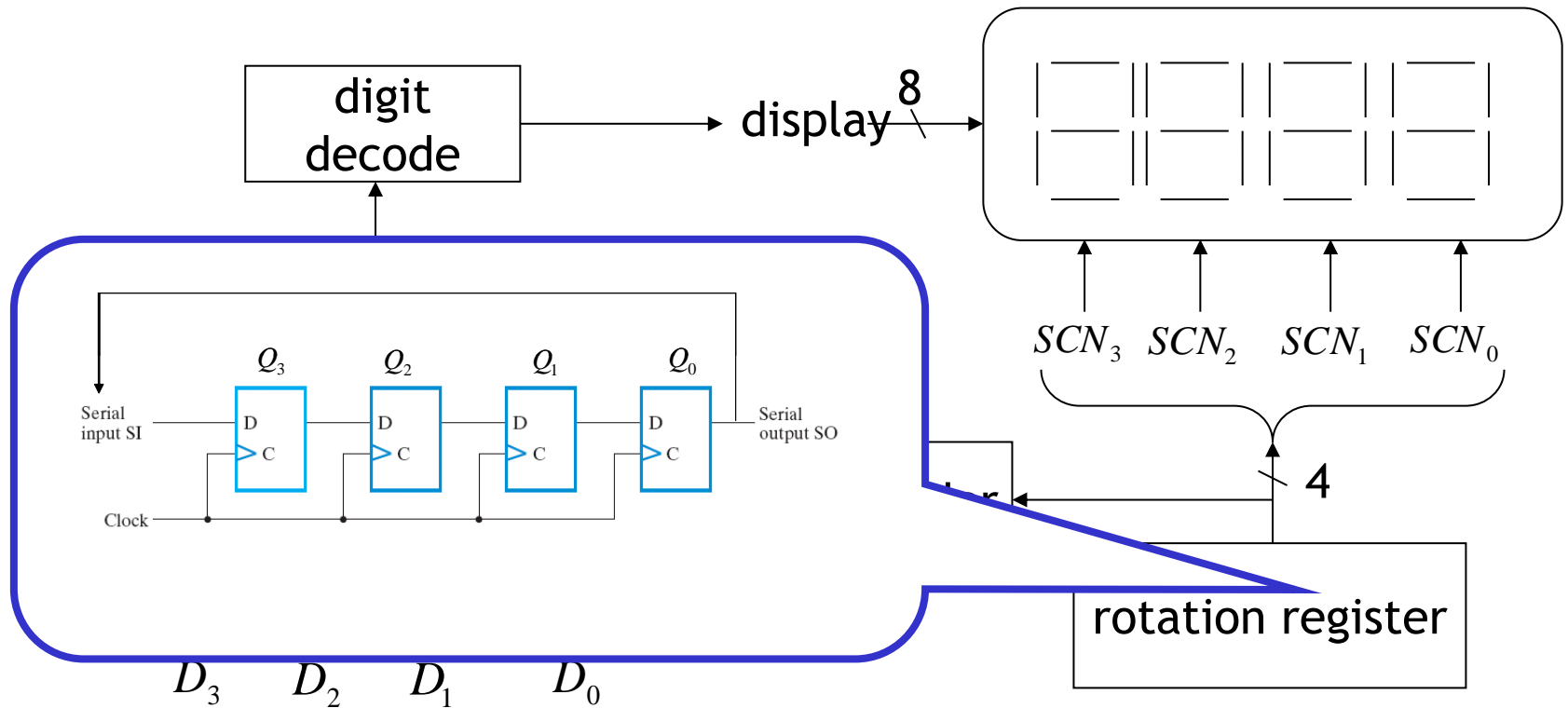

 
# Cooperation of rotation register and MUX control







# Rotation register to send SCN

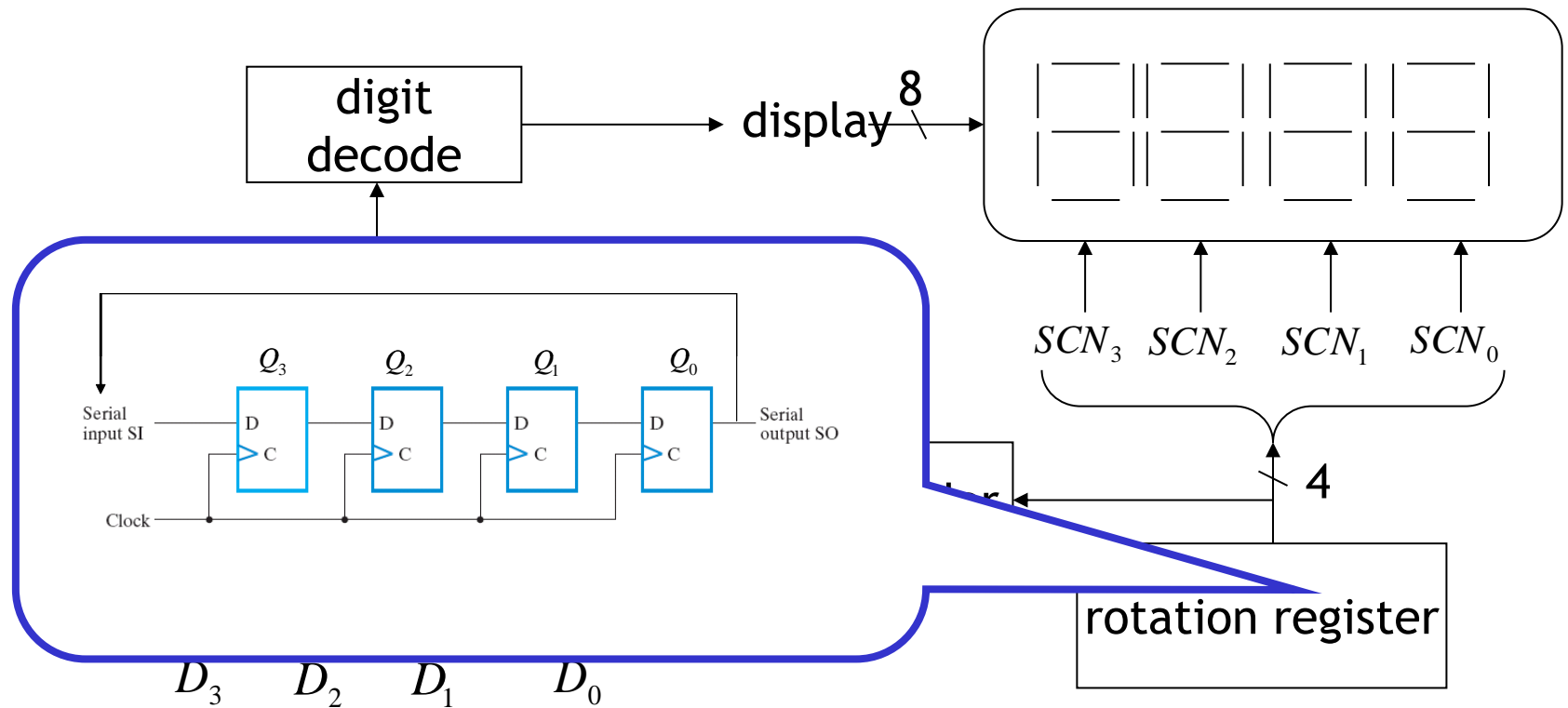


# Rotation register to send SCN

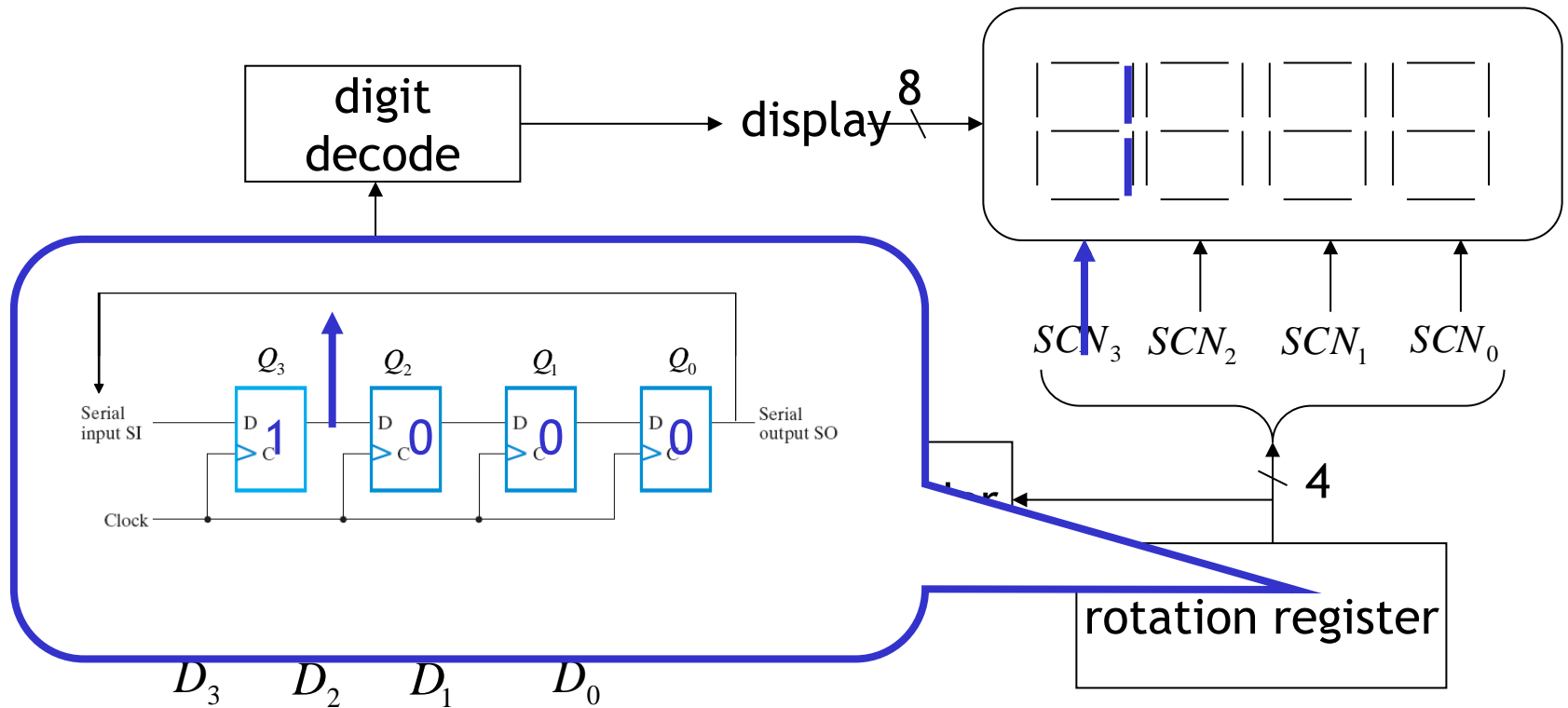


# Rotation register to send SCN

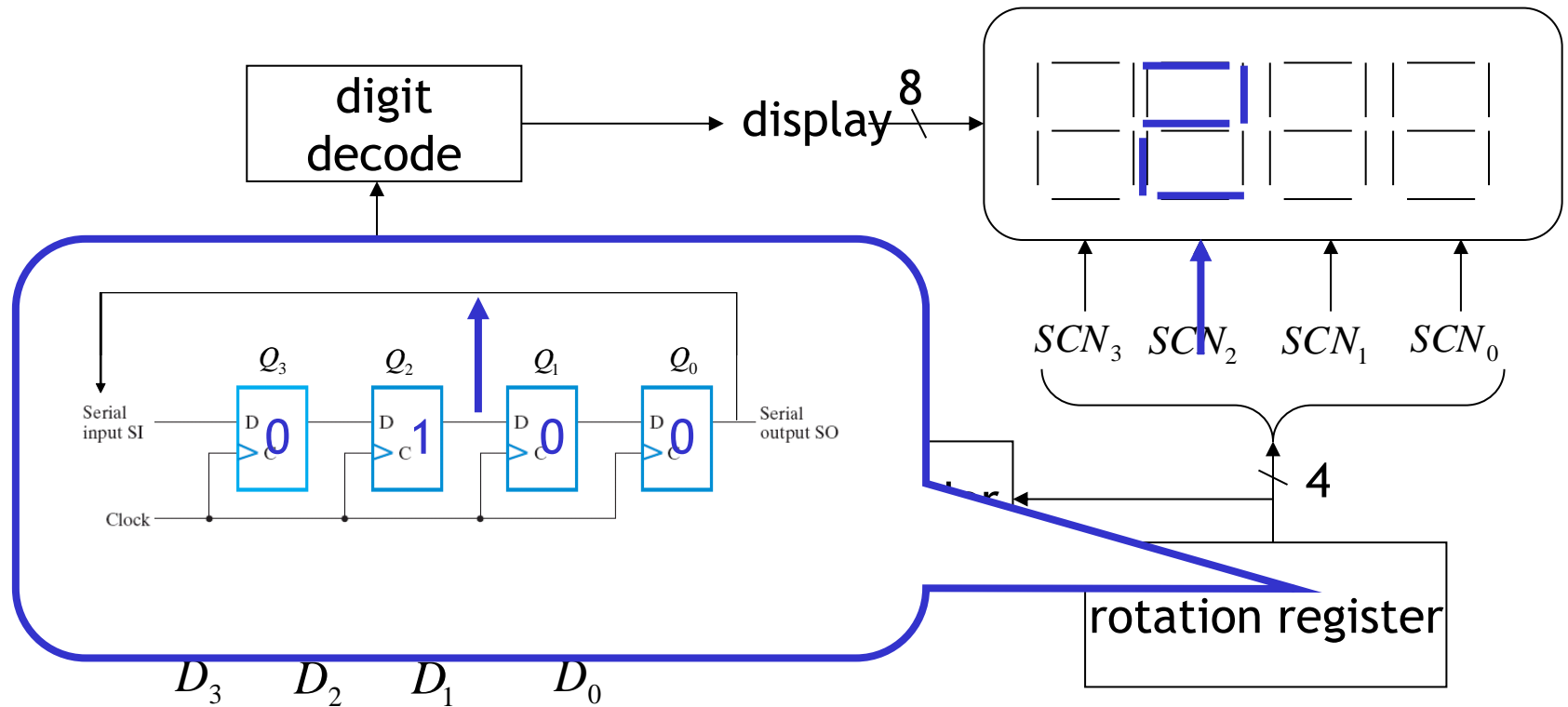


# Rotation register to send SCN

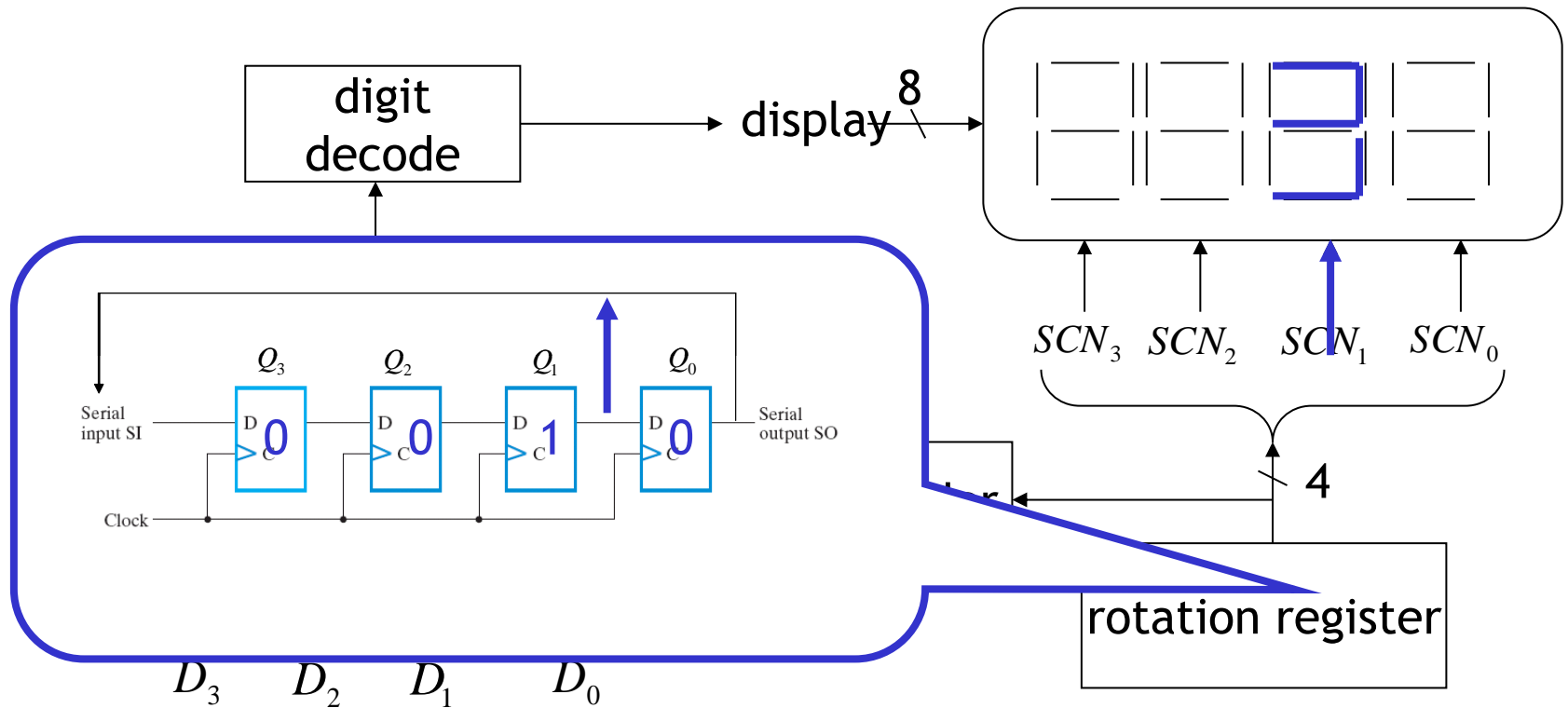


# Rotation register to send SCN

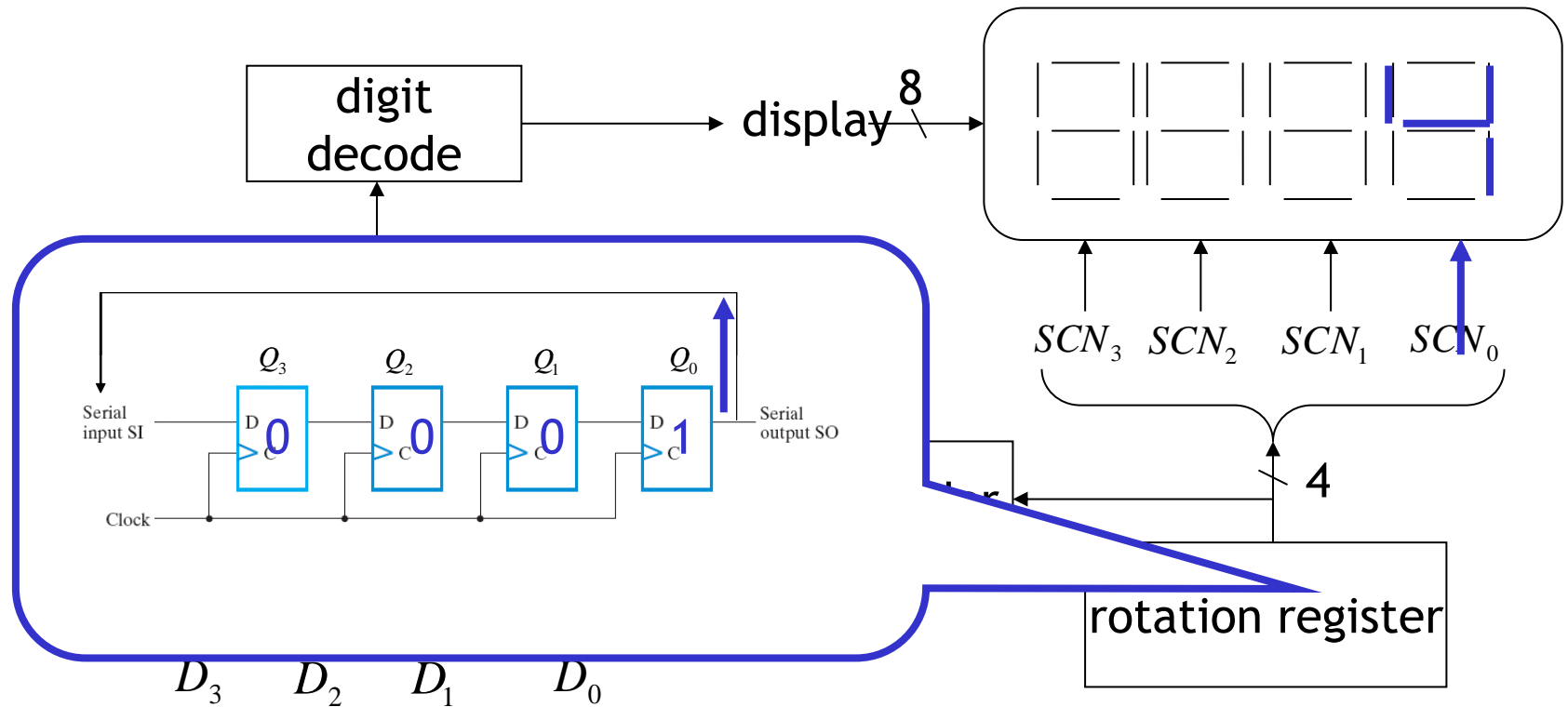


# Select display number by MUX

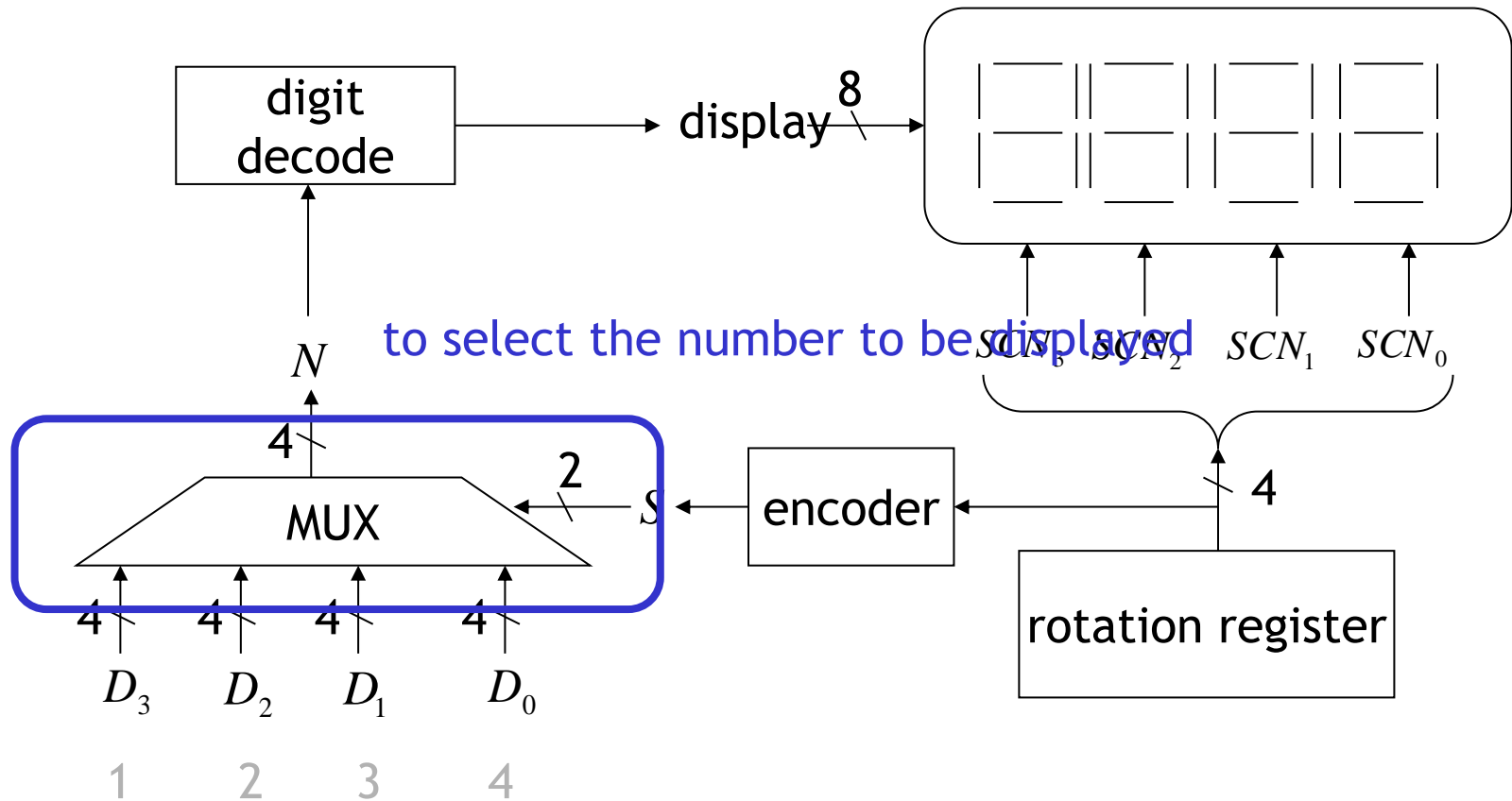

# Select display number by MUX

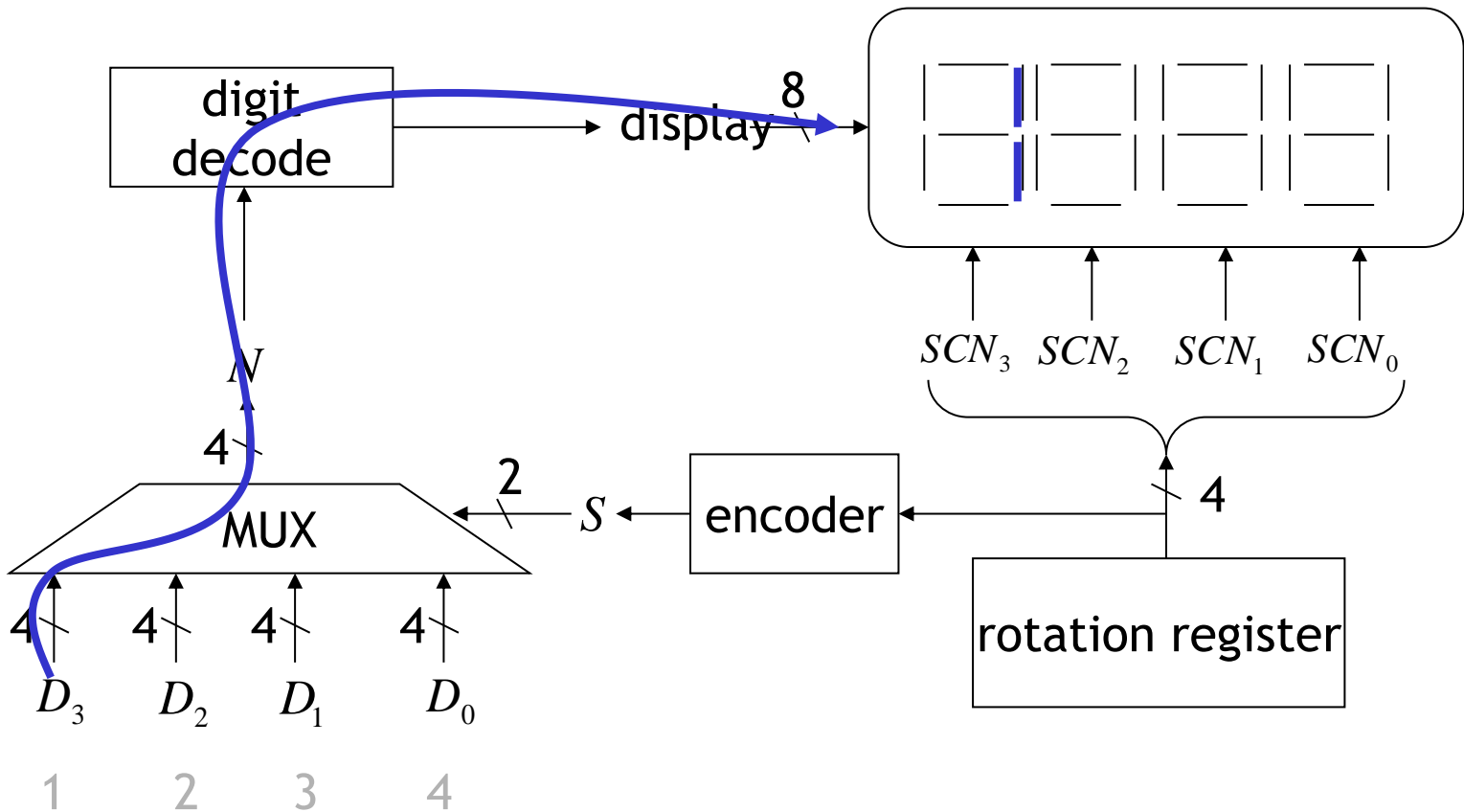


# Select display number by MUX

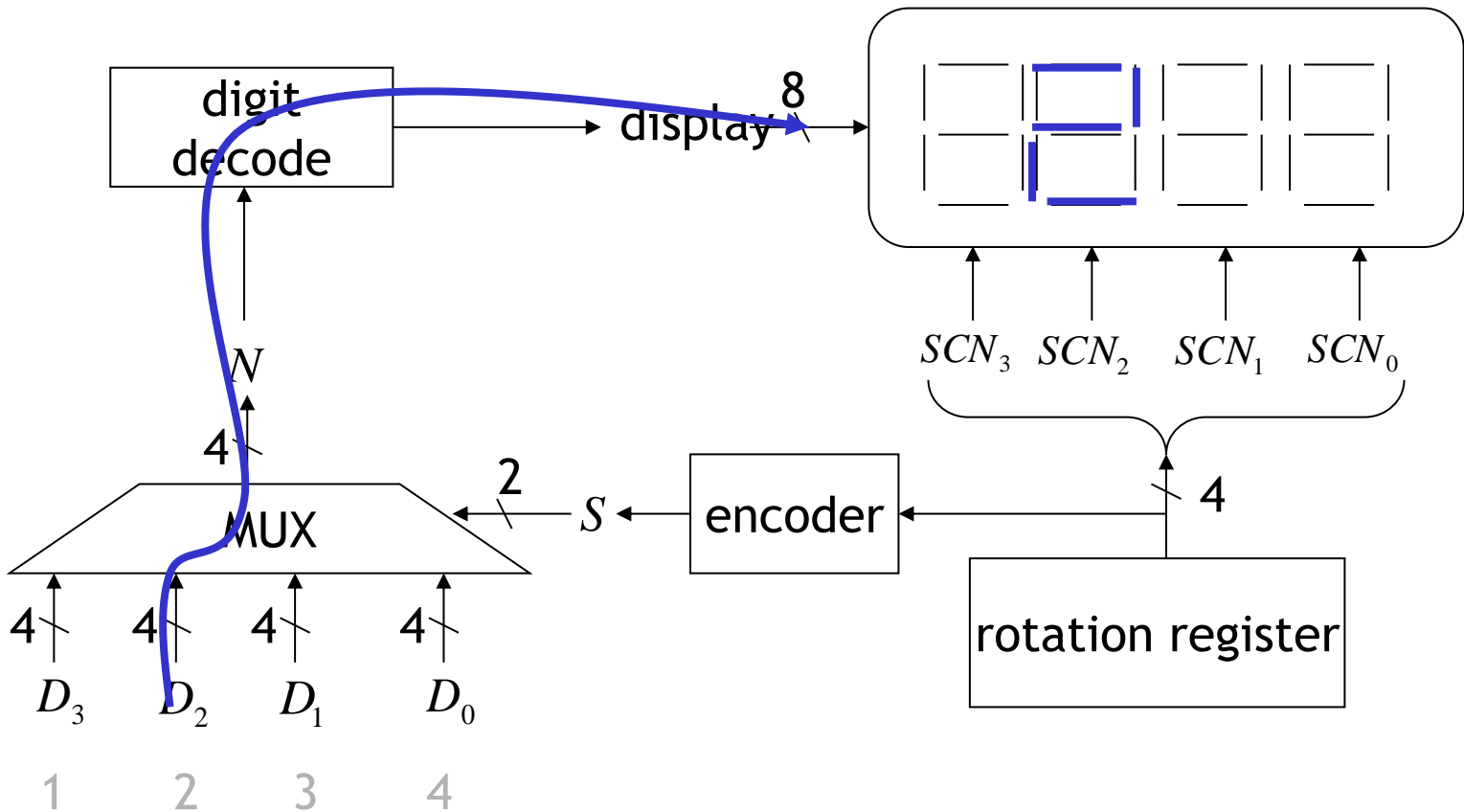





# Select display number by MUX

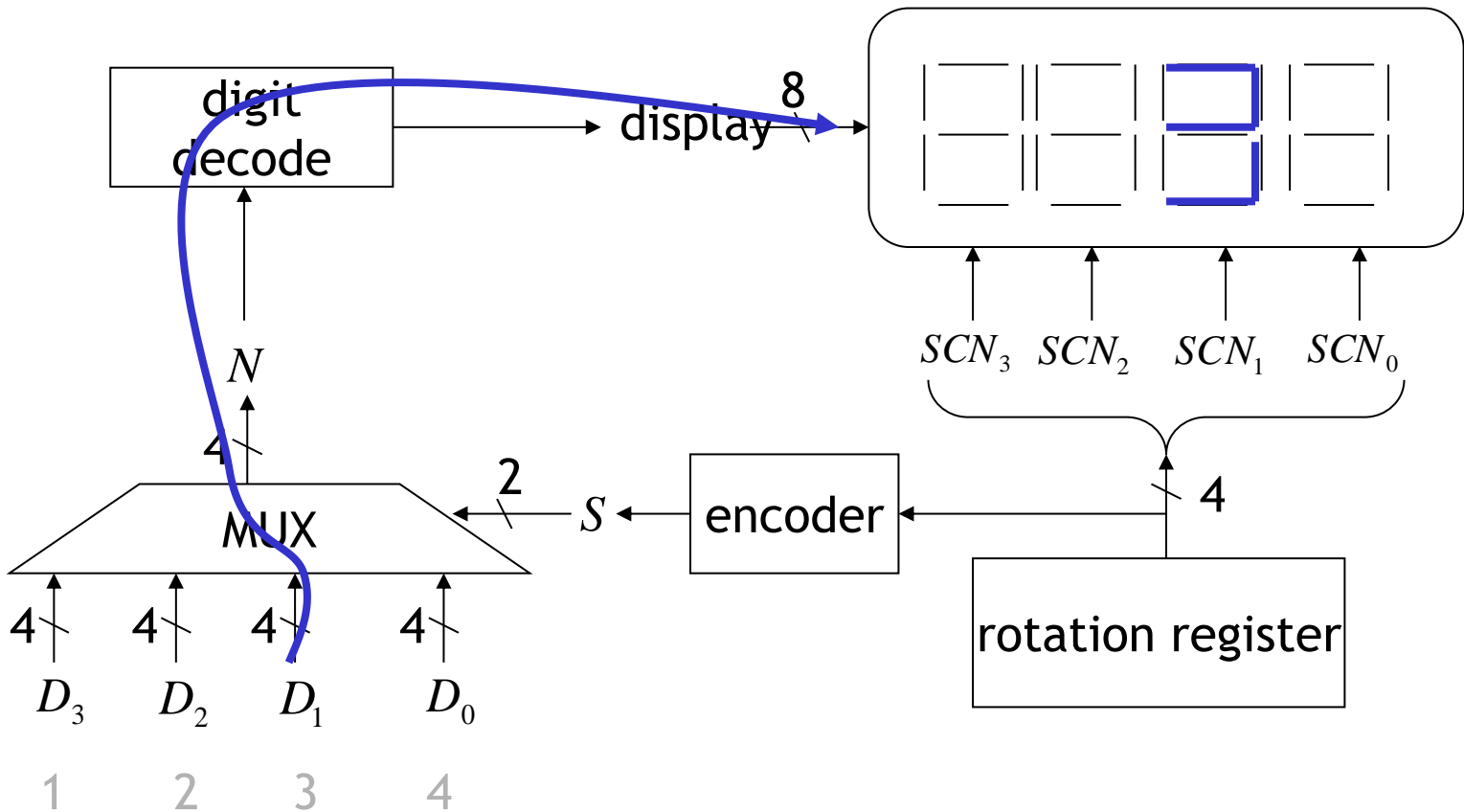



# Select display number by MUX

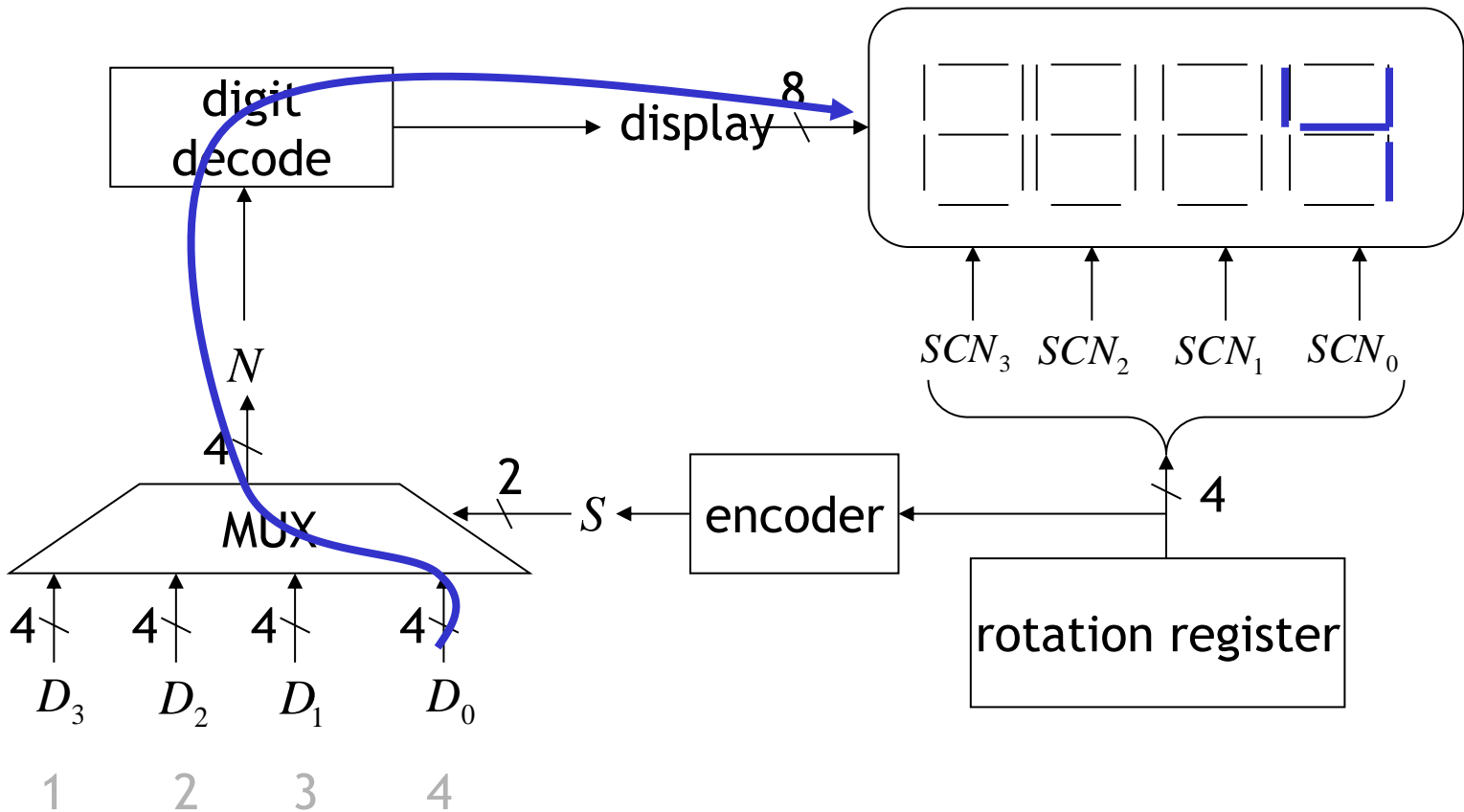

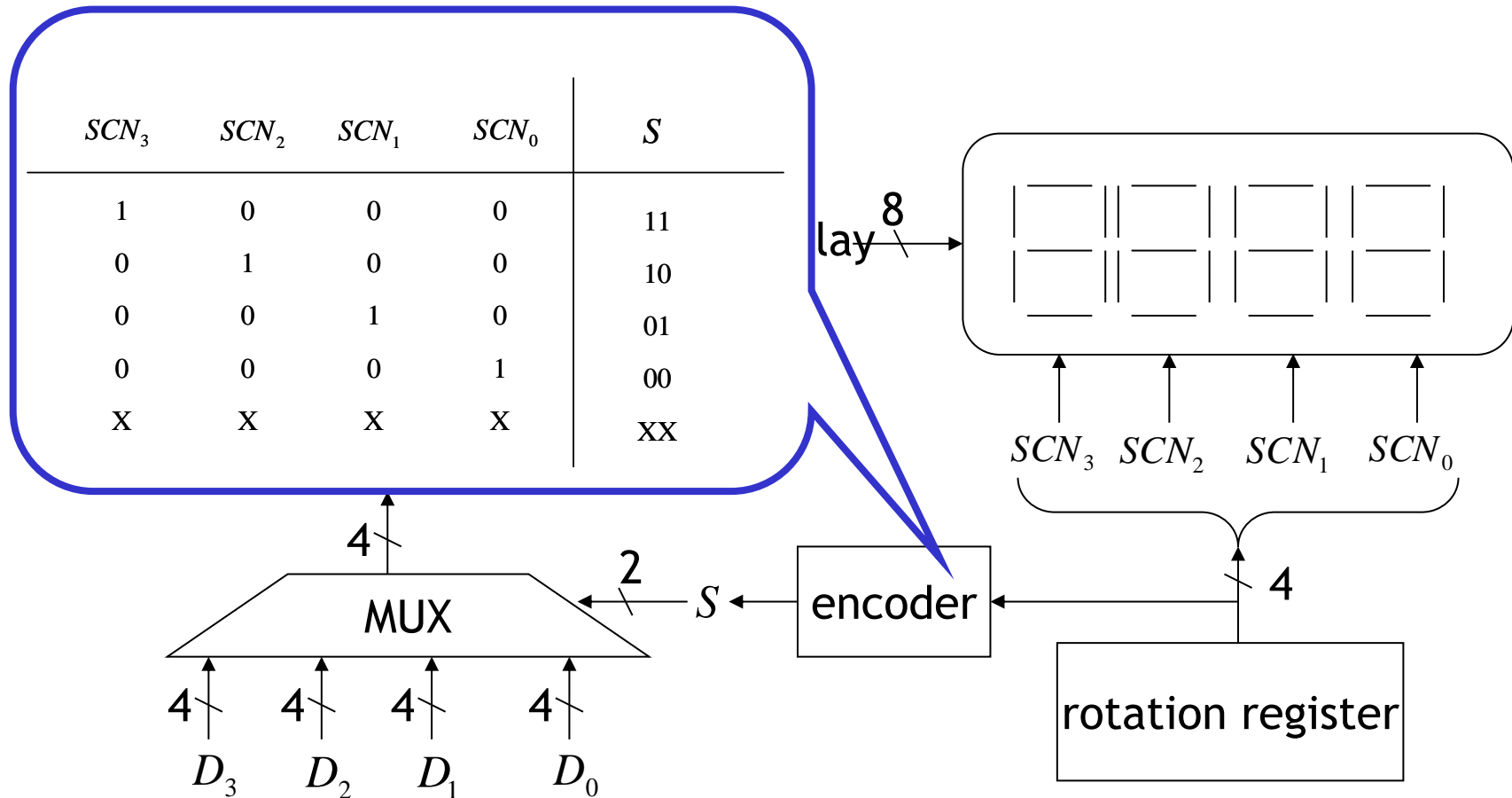
# Cooperation of rotation register and MUX control




# Timing Diagram

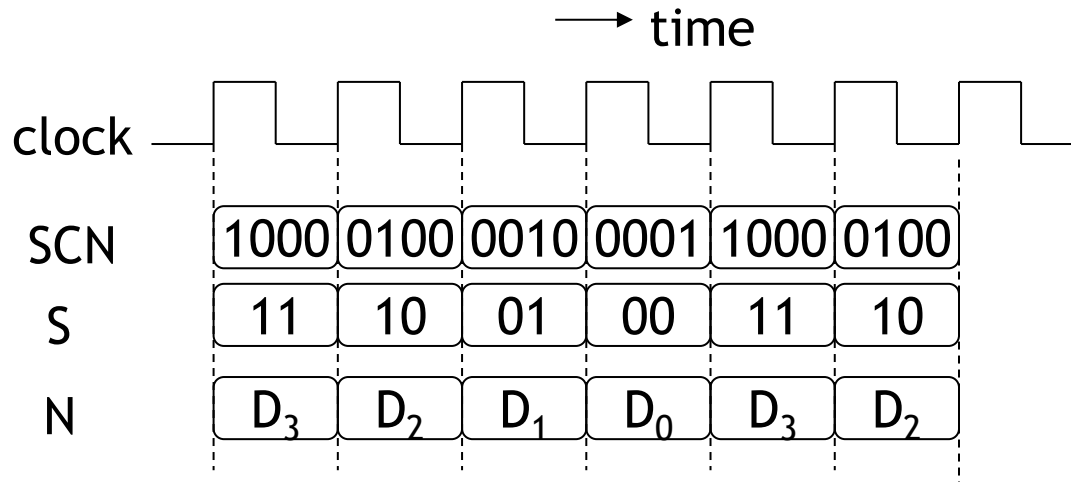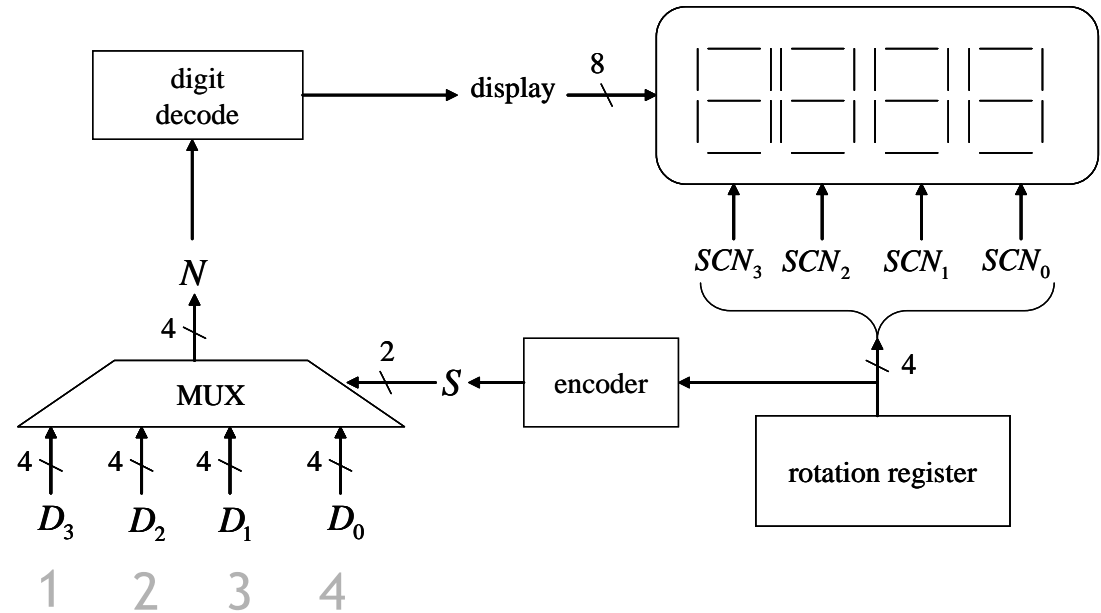

# Timing Diagram

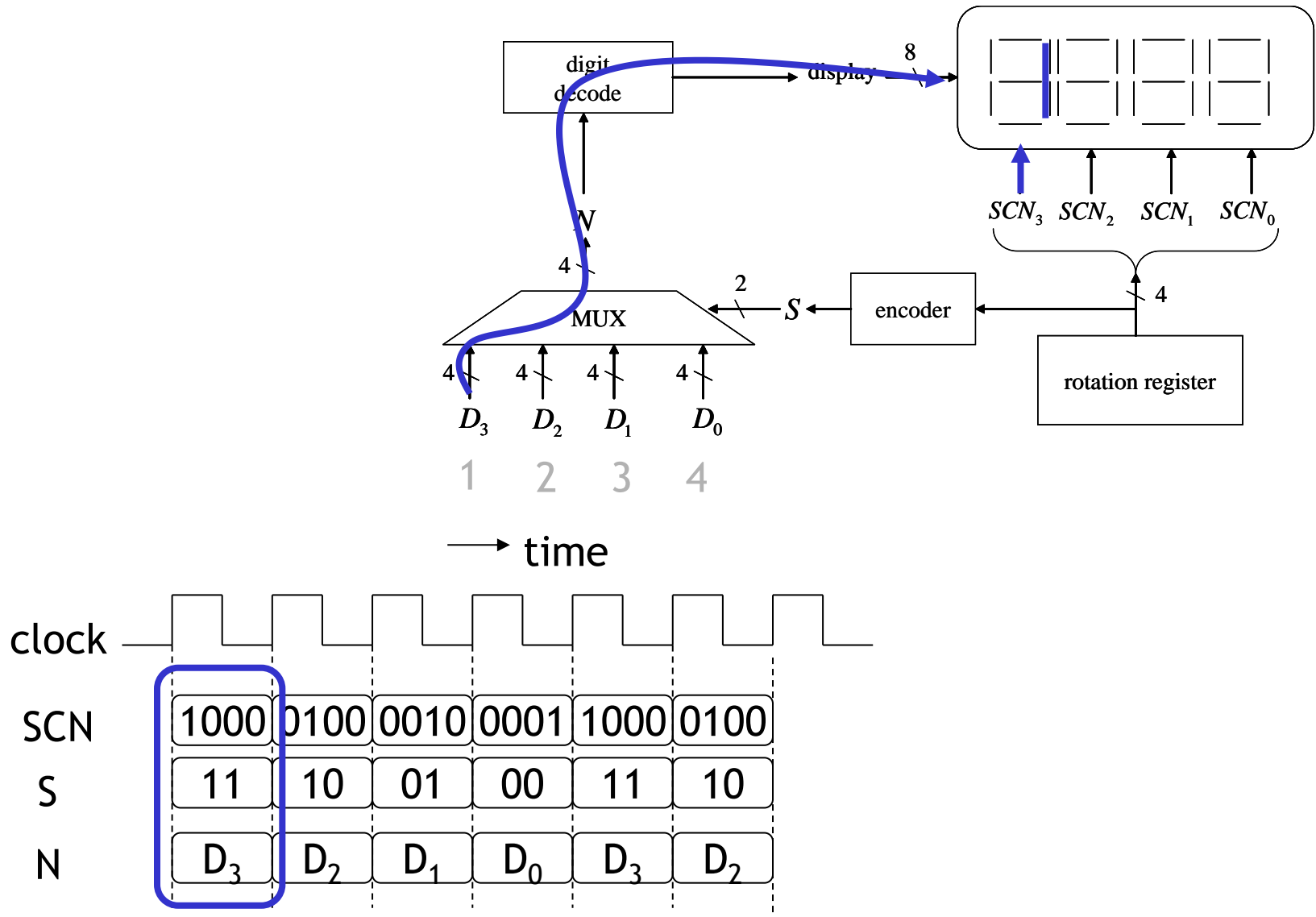

# Timing Diagram

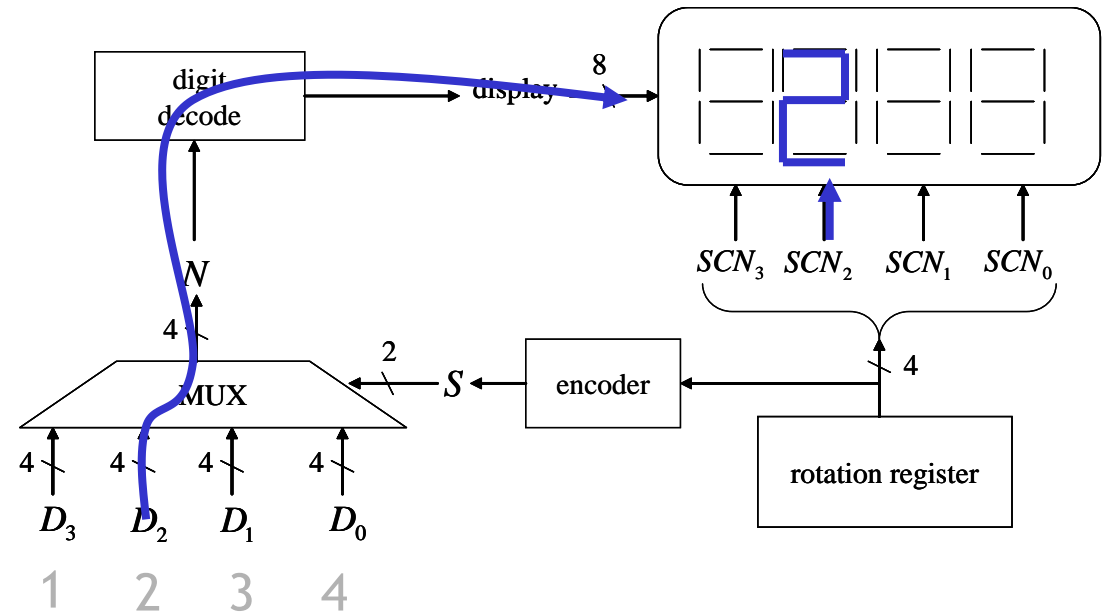

→ time

